

# VHDL Language

Design and synthesis of digital systems

**V. Fischer**

# Contents

- ⊕ ***Introduction***
- ⊕ ***VHDL basics***
- ⊕ ***Concurrent structures***
- ⊕ ***Applications of the concurrent structures***
  - decoders, parity checkers, multiplexers, arithmetic logic units, comparators, tri-state outputs, bi-directional inputs/outputs
- ⊕ ***Sequential structures***
- ⊕ ***Applications of the sequential structures***
  - latches, registers, counters
- ⊕ ***State machines***
- ⊕ ***Modularity and parameterization of modules***
- ⊕ ***Testbenches***



## Further reading

- ⊕ *Digital system design with VHDL*, Mark Zvolinski, Prentice Hall
- ⊕ *VHDL Modeling for Digital Design Synthesis*, Yu Chin Hsu, Kevin F. Tsai, Jessie T. Liu, Eric S. Lin, Kluwer Academic Publishers
- ⊕ *A guide to VHDL*, Stanley Mazor, Patricia Langstraat, Kluwer Academic Publishers

## Internet Sources

- ⊕ <http://www.2dix.com/pdf-2010/vhdl-synthesis-pdf.php>
- ⊕ <http://rdsg.epfl.ch/webdav/site/rdsg/shared/GR-SAN/vhdl-tutorial.pdf>
- ⊕ [http://www.mrc.uidaho.edu/mrc/people/jff/vhdl\\_info/Synthesis\\_Art\\_2P.pdf](http://www.mrc.uidaho.edu/mrc/people/jff/vhdl_info/Synthesis_Art_2P.pdf)
- ⊕ <http://web.ewu.edu/groups/technology/Claudio/ee360/Lectures/vhdl-for-synthesis.pdf>



# Description methods and languages

## ⊕ ***Classical description tool of the designer: schematic diagram***

- Uses logic gates or standard logic blocks
- Can contain several hierarchical levels: too complicated for complex digital systems

## ⊕ ***Description languages – textual tools offering:***

- More flexibility
- Larger variety of description techniques

## ⊕ ***First languages - PALASM, ABEL - equation-based languages:***

- Set of equations describing dependence of outputs on inputs of the block
- Sometimes supporting state machine design, too (ABEL)



## Description methods and languages (cont.)

### ⊕ ***Second generation of description languages:***

- Higher-level structures enabling description of the combinatorial and sequential systems using a behavioral approach (structures commonly used in scientific languages)

Example: ALTERA proprietary hardware description language (AHDL)

### ⊕ ***Third generation of description languages - VHDL, Verilog***


Two important evolutions:

- Technology-independent: used in multi-technology CAD systems (notion of retargeting and transportability)
- High abstraction level is especially well adapted to the design of complex digital systems

**VHDL** – VHSIC (Very High Speed Integrated Circuits) **H**ardware **D**escription **L**anguage
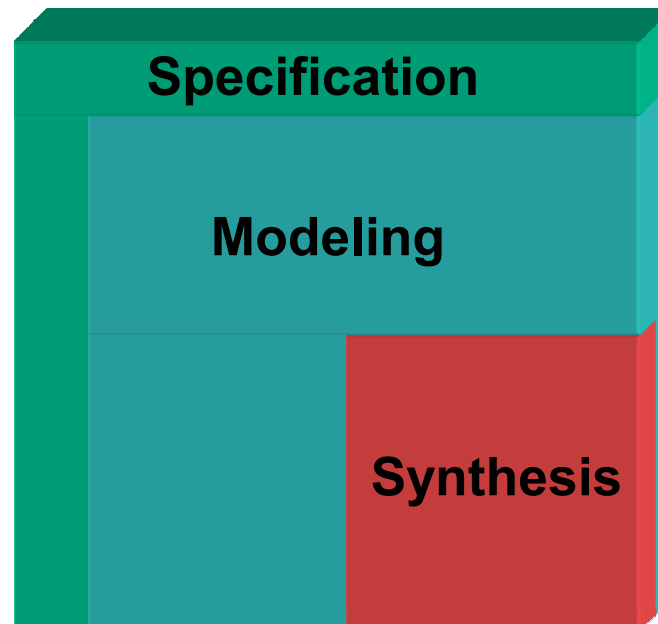
# Application of the system description using VHDL

- ⊕ **Specification** – specification of the system behavior
- ⊕ **Modeling** – functional verification by a simulation
- ⊕ **Synthesis** – physical realization in hardware



- ⊕ **Synthesizable structures represent a subset of the VHDL language**

**Conclusion :**

**Structures that can be modeled (simulated) are not necessarily synthesizable!**



## Role of the simulation

⊕ **With the evolution of the system complexity the design methods have changed:**

- Hardware prototyping has been gradually replaced by the simulation - it enables to reduce the cost and the development delays and to design high-level digital systems
- Simulation is used in all development phases of the digital system (specification, design and verification)



# Types of simulation


## ⊕ **Functional simulation:**

- Aim – formal functional verification of each element of the system
- Signal propagation delays are not considered, the simulated system is supposed to be perfect

## ⊕ **Timing (physical) simulation:**

- Aim – to get simulation results as close to the reality (behavior of the physical system) as possible, so
- Signal propagation delays are taken into account

# Digital system design flow

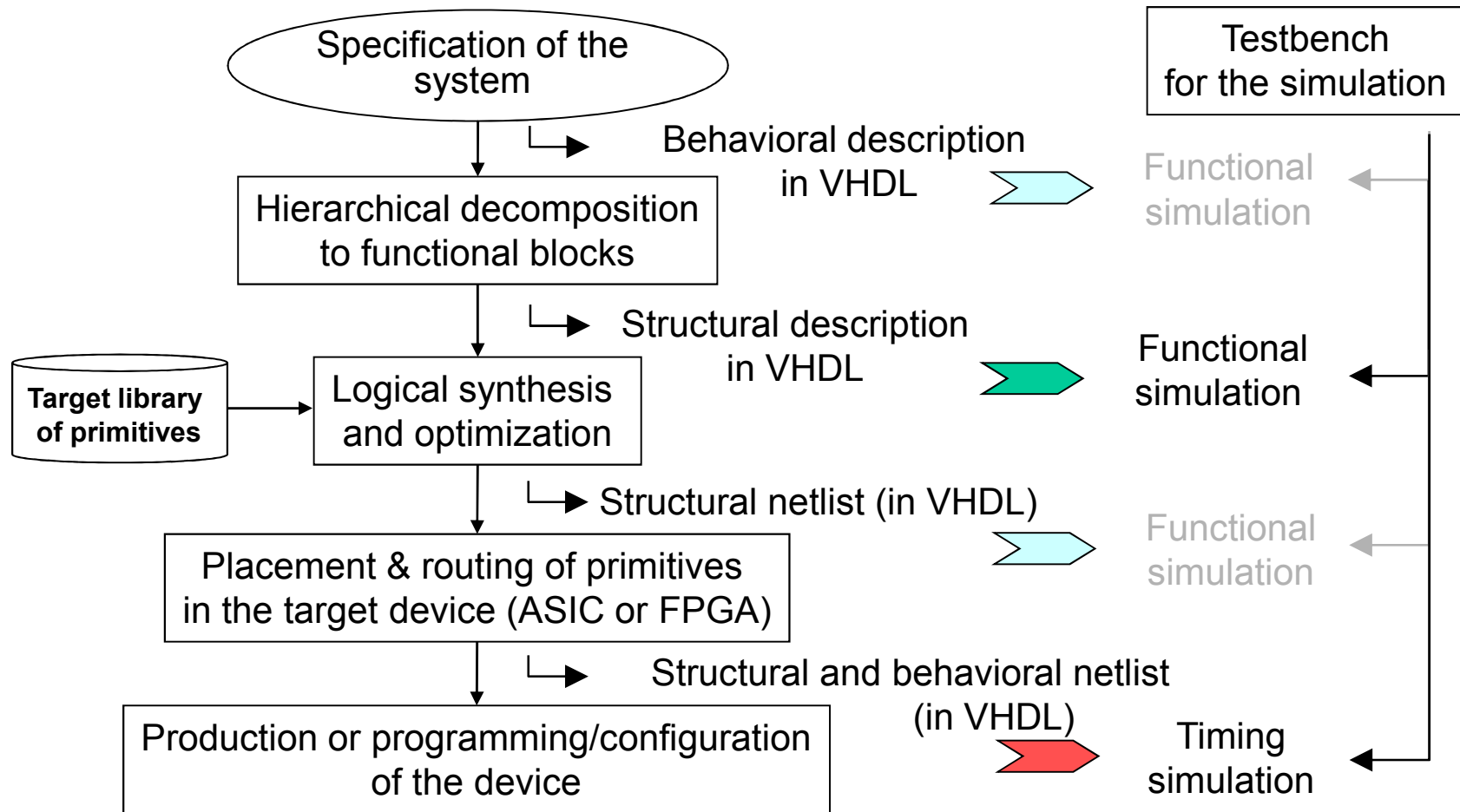

# Contents

- ⊕ ***Introduction***
- ⊕ ***VHDL basics***
- ⊕ ***Concurrent structures***
- ⊕ ***Applications of the concurrent structures***
  - decoders, parity checkers, multiplexers, arithmetic logic units, tri-state outputs, bi-directional inputs/outputs
- ⊕ ***Sequential structures***
- ⊕ ***Applications of the sequential structures***
  - latches, registers, counters
- ⊕ ***State machines***
- ⊕ ***Modularity and parameterization of modules***
- ⊕ ***Testbenches***

# Foreword

## ⊕ Characteristics of the VHDL language:

- Rich vocabulary
- Different contexts of utilization (specification, modeling, synthesis)

## ⊕ Two important aspects of the VHDL language:

- VHDL – a **description language** aimed at description/simulation of logic systems, it is NOT a programming language
- Some elements of the language **cannot be used in all application contexts**

## ⊕ Note:

In the following sections, we'll use a subset of the VHDL language – basic structures used to synthesize digital systems!

# VHDL design units


VHDL description is composed of design units. A design unit represents a subset of the logic structure that can be compiled separately, saved in an independent file or in a library. It can be situated in a:

- file \*.vhd (also several units in one file)
- (working) directory in several files \*.vhd
- library (packet)

## ⊕ Design units:

- **entity** – basic element (component, module) defined by:
  - entity specification (= external interface ⇒ symbol)
  - architecture (= internal structure ⇒ schematics)
- **packet** – grouping of elements defined by
  - packet specification– list of objects belonging to the packet
  - packet body – description (definition) of each object
- **configuration** – association of an architecture with an entity

# Entity specification

 


## ⊕ **Design entity – basic construction element:**

- From an external point of view, it is specified by **input/output signals**
- From an internal point of view, it is specified by the **architecture**
- One entity can have several **architectures** (several versions of the internal structure)
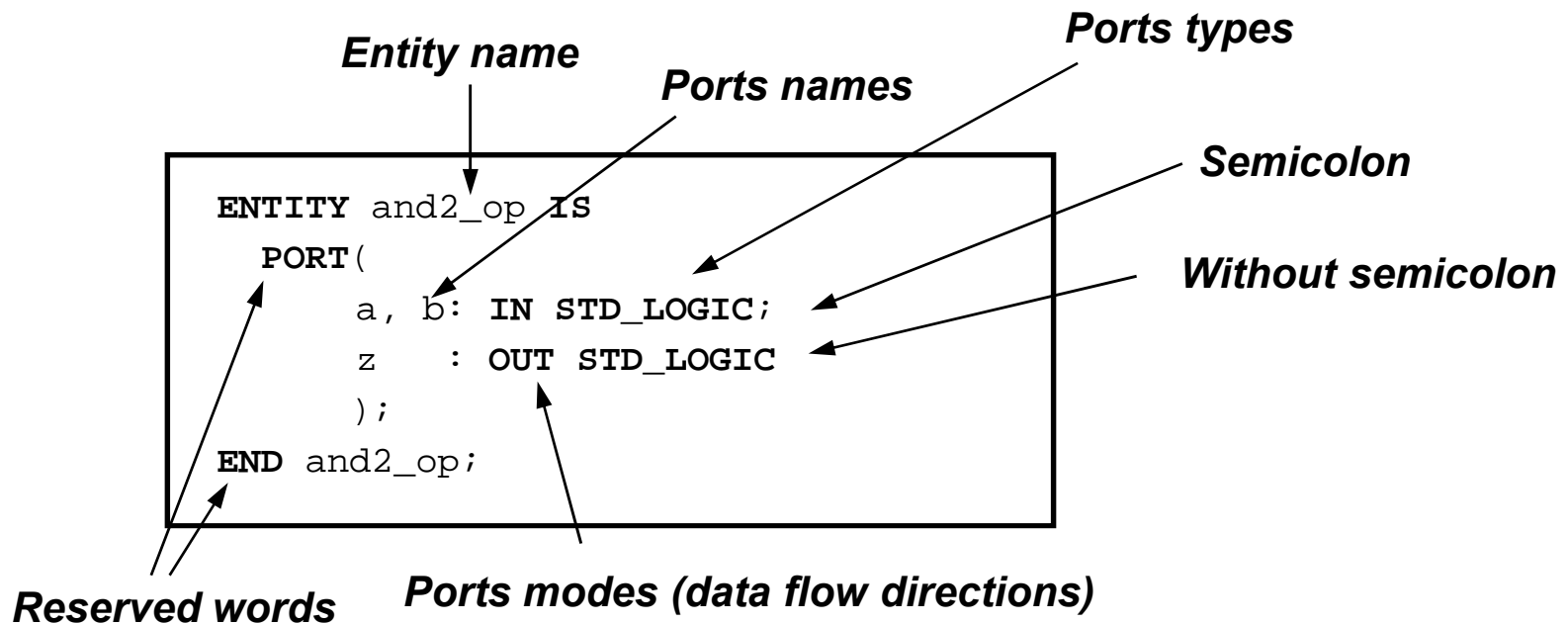
# Entity declaration


- ⊕ Describes the name, the parameters and the interface (input/output signals) of the component




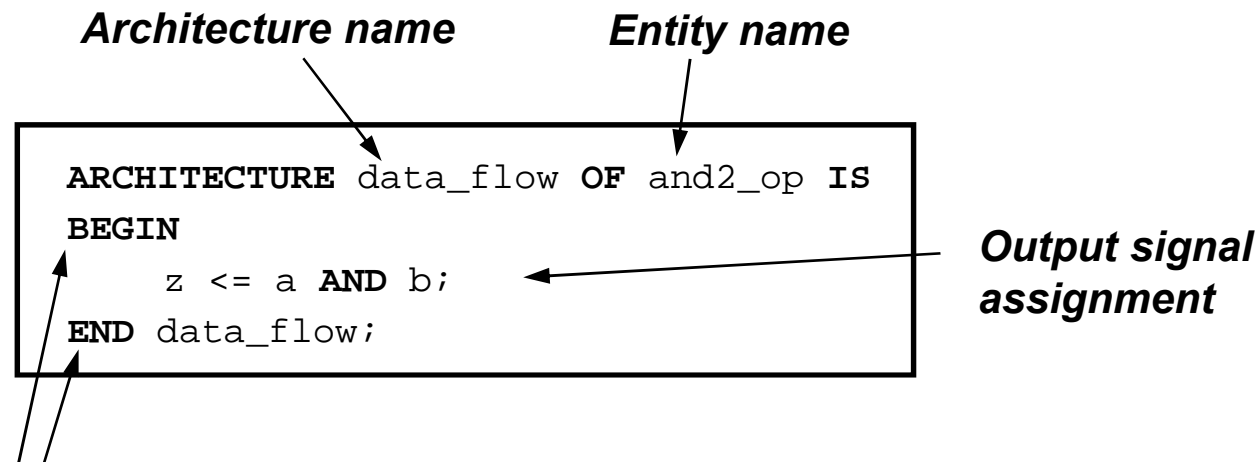
# Architecture description

- ⊕ **Architecture** - describes component implementation by a
  - **Data flow** description model
  - **Structural** description model
  - **Behavioral** description model



*Reserved words delimiting  
the architecture*



# Entity and architecture declaration


## ⊕ *Complete description of the logic structure*

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;


ENTITY and2_op IS
    PORT(
        a, b: IN STD_LOGIC;
        z   : OUT STD_LOGIC);
END and2_op;

ARCHITECTURE data_flow OF and2_op IS
BEGIN
    z <= a AND b;
END data_flow;
```

# Port mode **IN**

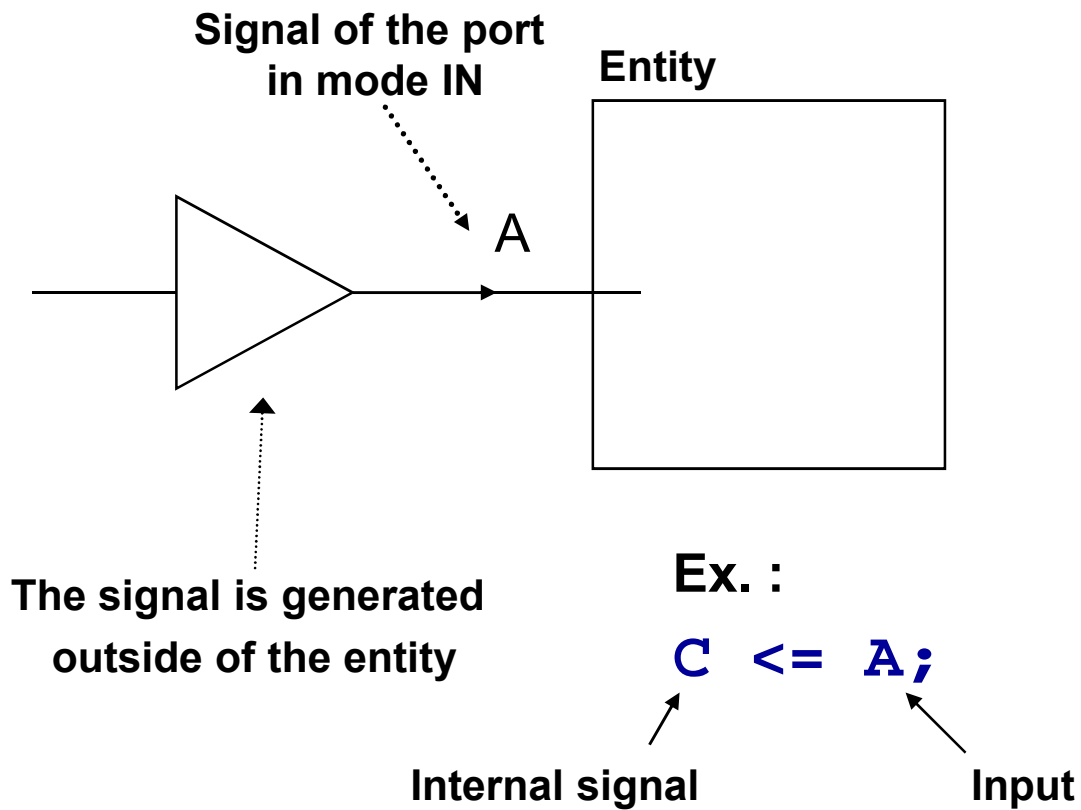


# Port mode **OUT**

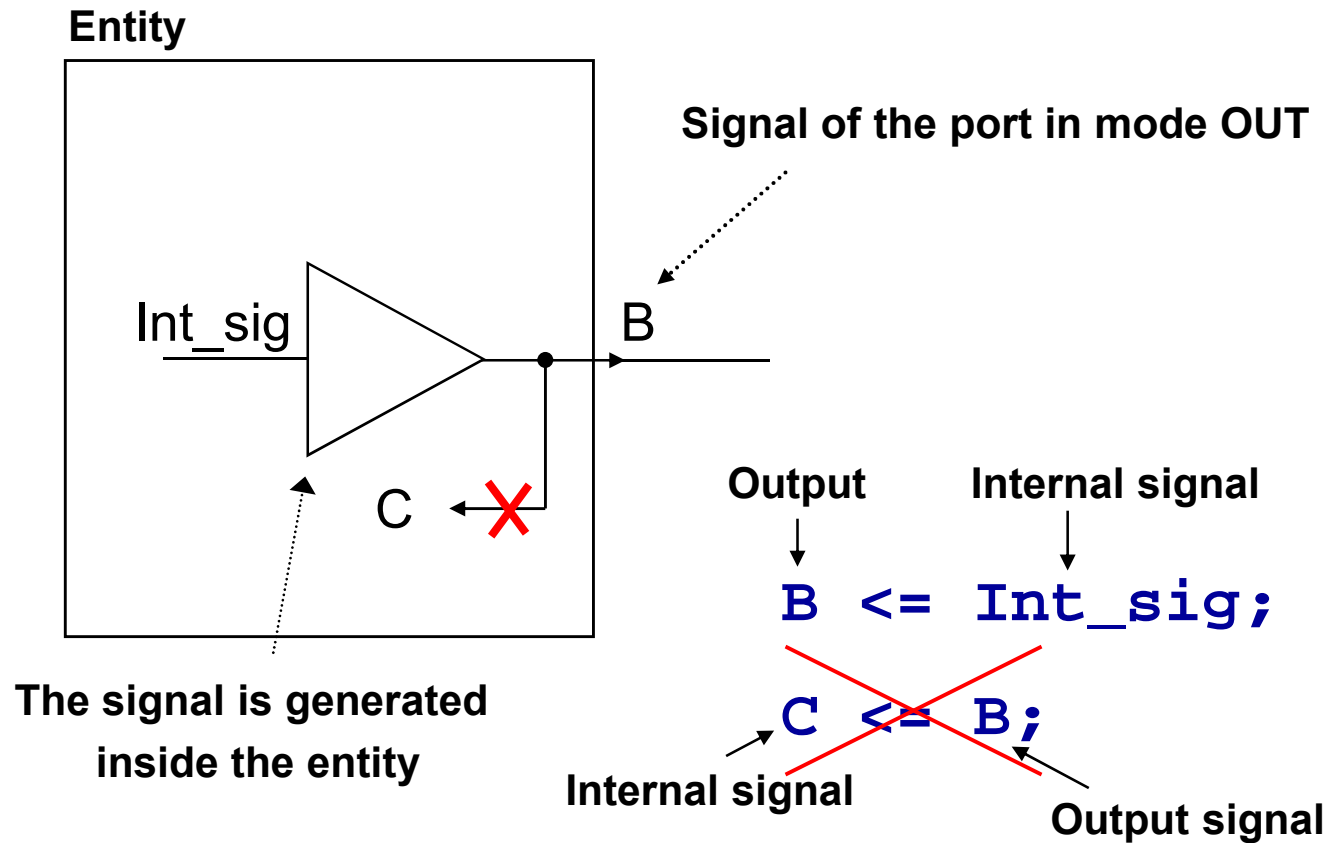

**Problem:** the signal in the mode OUT cannot be read (referenced) inside the entity (C cannot read B in mode OUT)

## Port mode **BUFFER**

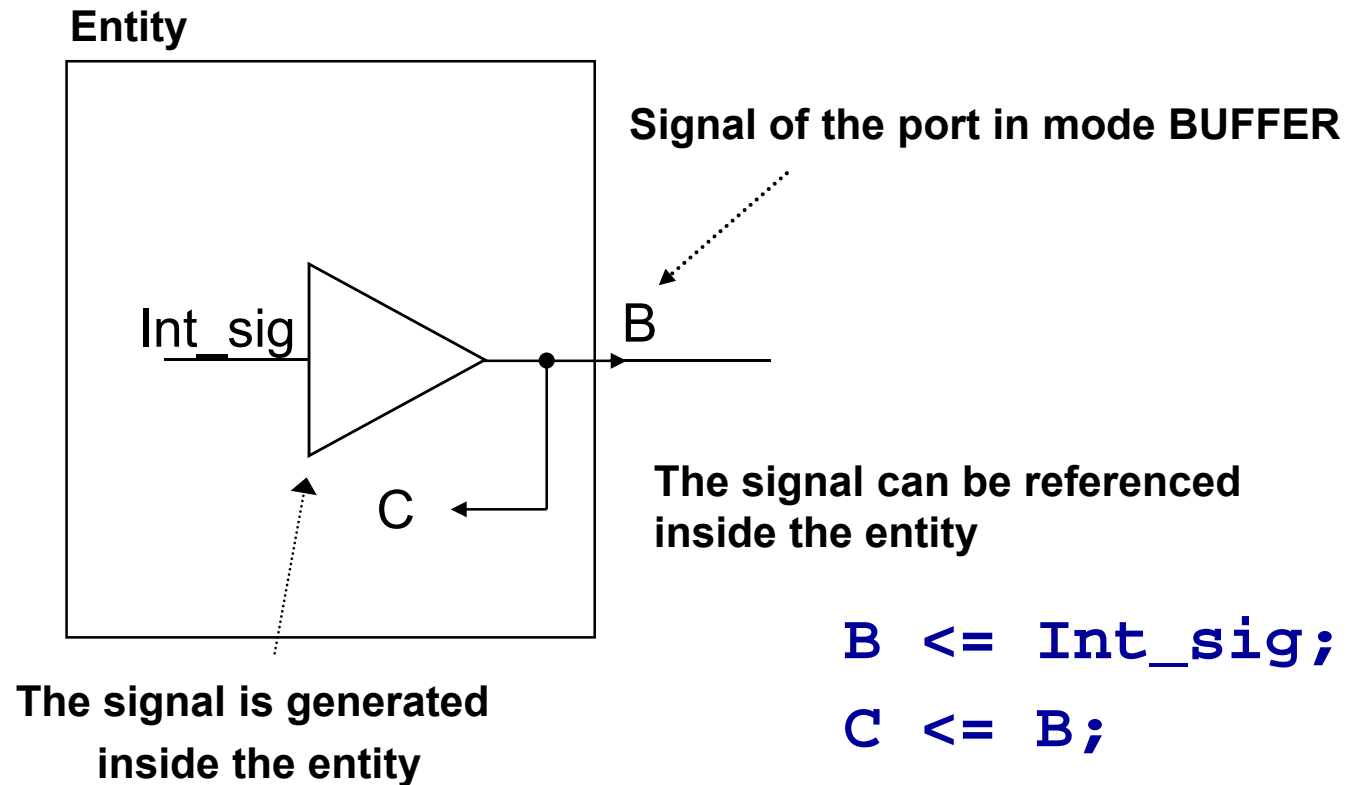


**Problem:** the output signal in the mode **BUFFER** cannot be connected to a port in the mode **OUT** in the higher hierarchical level

## Port mode **BUFFER** (cont.)


Superior entity

Entity

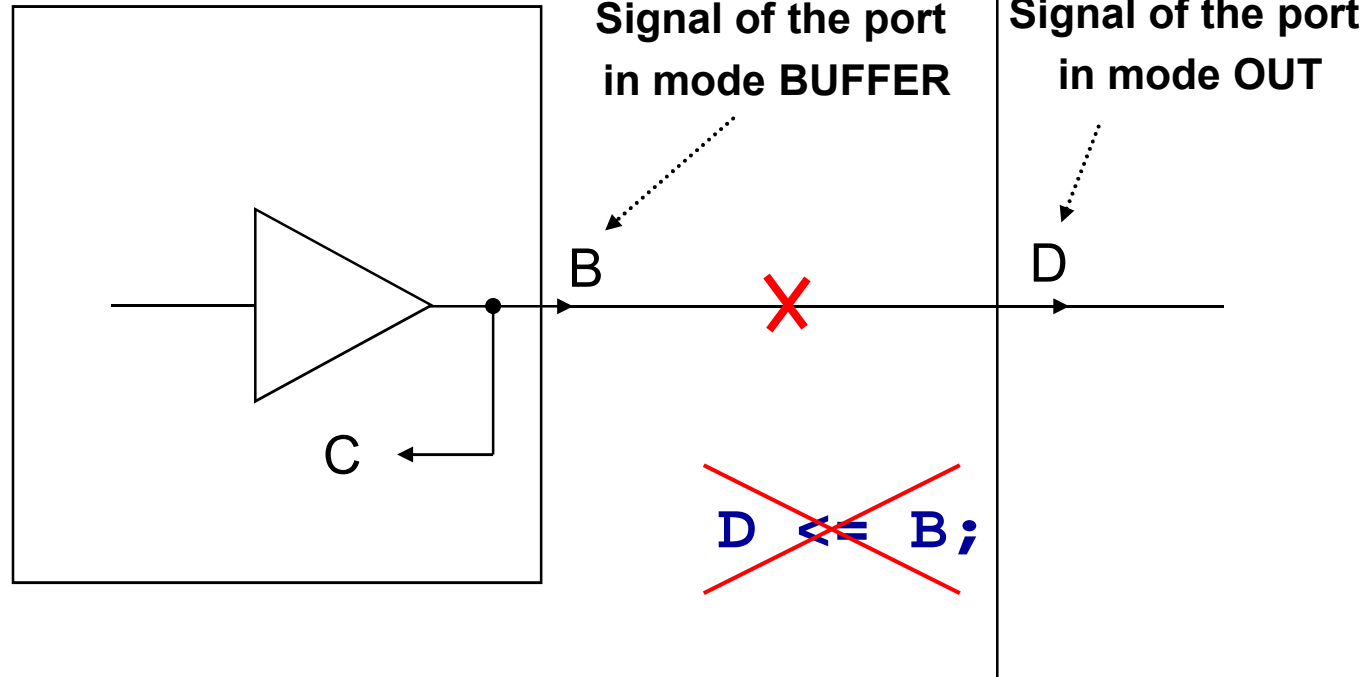


**Solution:** see the next slide
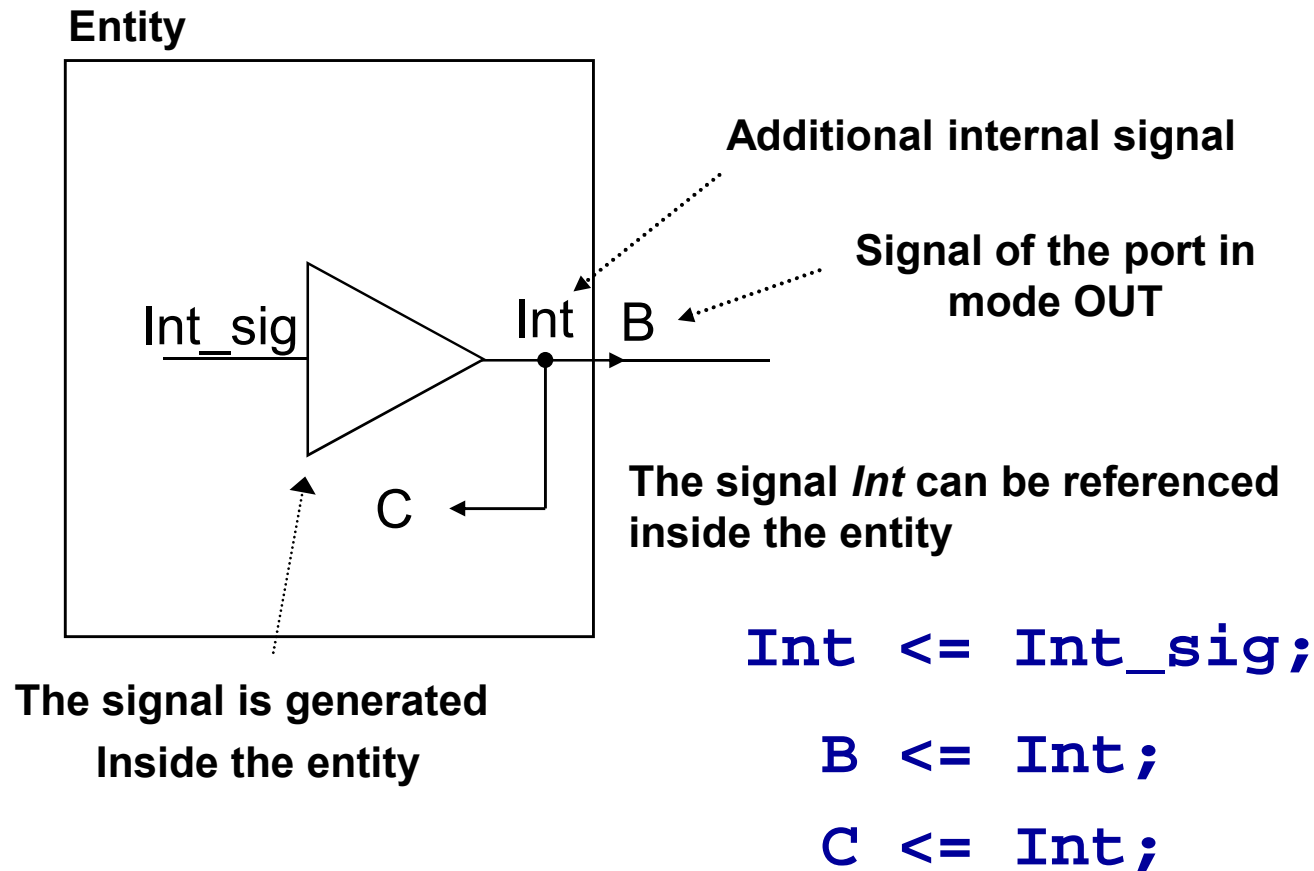
## Port mode **OUT** with an **internal signal**



## Port mode **INOUT** (bi-directional)

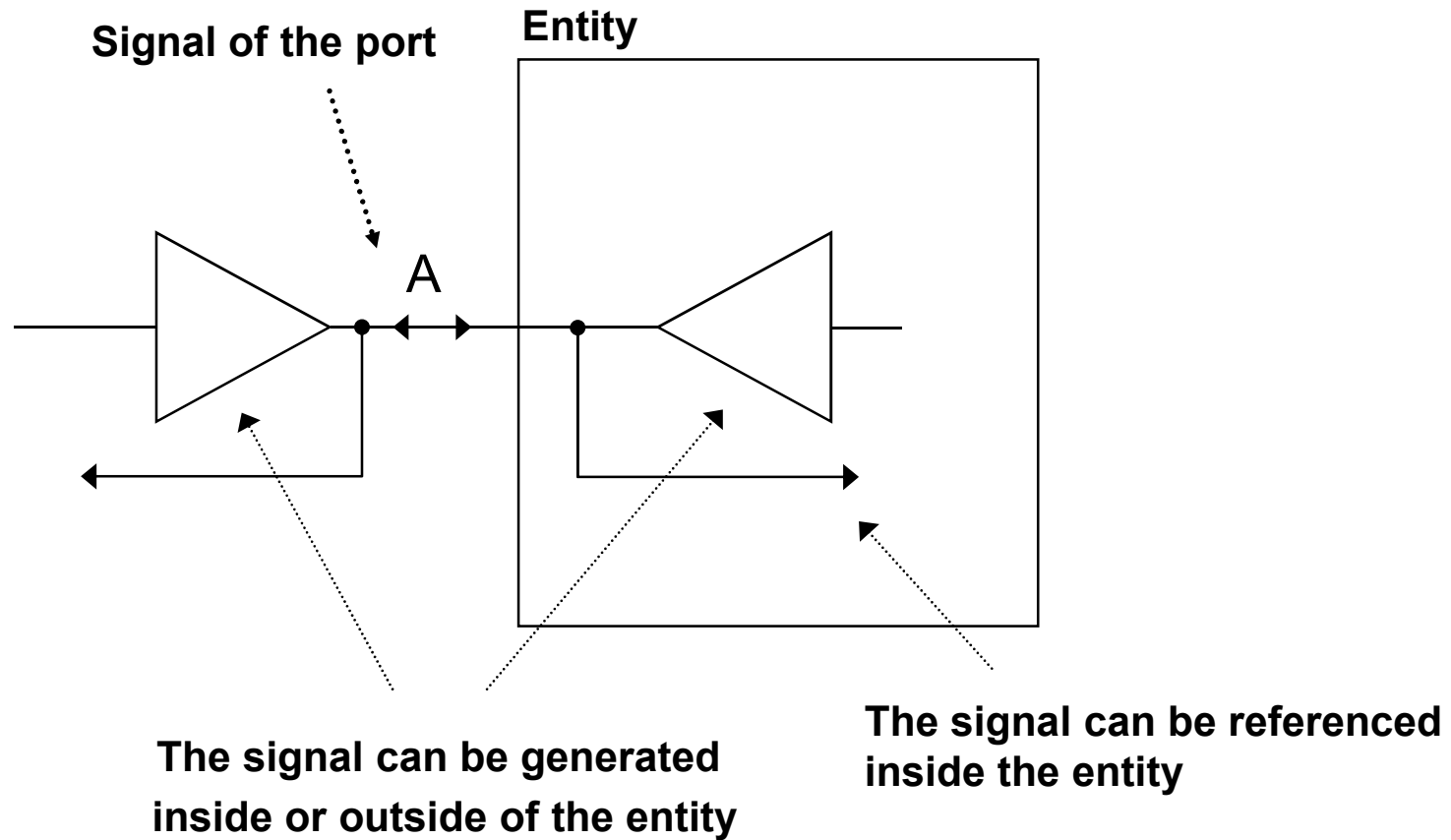

## Port modes - summary

⊕ ***Modes of the ports specify the direction of the data transfer (when looking from the component side)***

- **IN**: input port – data coming to this port can be read inside the component, the name of the port can be situated **only on the right side** of the assignment expression
- **OUT**: output port – output data can only be updated (and not read) inside the component, the name of the port can be situated **only on the left side** of the assignment expression
- **INOUT**: input/output port – data can be updated and read inside the component, the name of the port can be situated **on the left or on the right side** of the assignment expression
- **BUFFER**: output port – output data can be read inside the component, the name of the port can be situated **on the left or on the right side** of the assignment expression, this mode should be avoided in the hierarchical structures



# Data types

- ⊕ ***Type – specifies the data format and the set of operations, which are allowed on these data***
- ⊕ ***Two categories***
  - **Scalar data types**
    - Integers
    - Real numbers (floating point)
    - Physical data (measure units)
    - Enumerated data (an explicit list of data)
  - **Composite data types**
    - Arrays (groups of objects of the same type)
    - Records (aggregates of objects of different types)

# Data types

## ⊕ Pre-defined types (library STD)

scalar types	sim	syn	composite types (arrays)	sim	syn
<b>character</b> (enum)	✓	✓	<b>string</b>	✓	✓
<b>bit</b> (enum)	✓	✓	<b>bit_vector</b>	✓	✓
<b>boolean</b> (enum)	✓	✓			
<b>real</b> (float)	✓				
<b>integer</b> (integer)	✓	✓			
<b>time</b> (physical)	✓				

## ⊕ Types defined in the IEEE library

scalar types	sim	syn	composite types (arrays)	sim	syn
<b>std_ulogic</b>	✓		<b>std_ulogic_vector</b>	✓	
<b>std_logic</b> (signals)	✓	✓	<b>std_logic_vector</b> (signal vectors)	✓	✓

## ⊕ User-defined types

*Note: ulogic = unresolved logic (non-resolved multi-value signals = mono-source)*

# Unresolved versus resolved logic

## ⊕ **Unresolved logic** – *std\_ulogic*

- **Mono-source signals** – only one driver can generate one signal
- Ensures that two different values will not be assigned to a signal on two different places
- Tri-state buses cannot be implemented (need two generators for the same signal)

## ⊕ **Resolved logic** – *std\_logic*

- **Multi-source signals** – several generators can generate one signal
- Used for implementation of bi-directional signals (e.g. buses)
- A **conflict resolution table** is given in the IEEE library (ex. : '0' and '1' give 'X', 'Z' and '1' give '1', etc.)

Attention on multiple signal assignments when using resolved logic inside the same architecture – this error will not be signaled by the compiler (more than one generator is allowed)!

## Type STD\_LOGIC (multi-value, multi-source signals)


Value	Meaning	Simul.	Synth.
'U'	<i>Unknown</i> – non initialized	✓	
'X'	<i>Forcing unknown</i> – unknown level, strong forcing	✓	
'0'	<i>Forcing 0</i> – level 0, strong forcing	✓	✓
'1'	<i>Forcing 1</i> – level 1, strong forcing	✓	✓
'Z'	<i>High Impedance</i> – high impedance	✓	✓
'W'	<i>Weak Unknown</i> – unknown level, weak forcing	✓	
'L'	<i>Weak 0</i> – level 0, weak forcing	✓	
'H'	<i>Weak 1</i> – level 1, weak forcing	✓	
'-'	<i>Don't Care</i> – any level	✓	✓

## Meaning of the STD\_LOGIC levels

'U'


- Default signal value at the beginning of the simulation
- Value of signals, which are not generated (updated) during the simulation

'X'

 


## Meaning of the STD\_LOGIC levels (cont.)

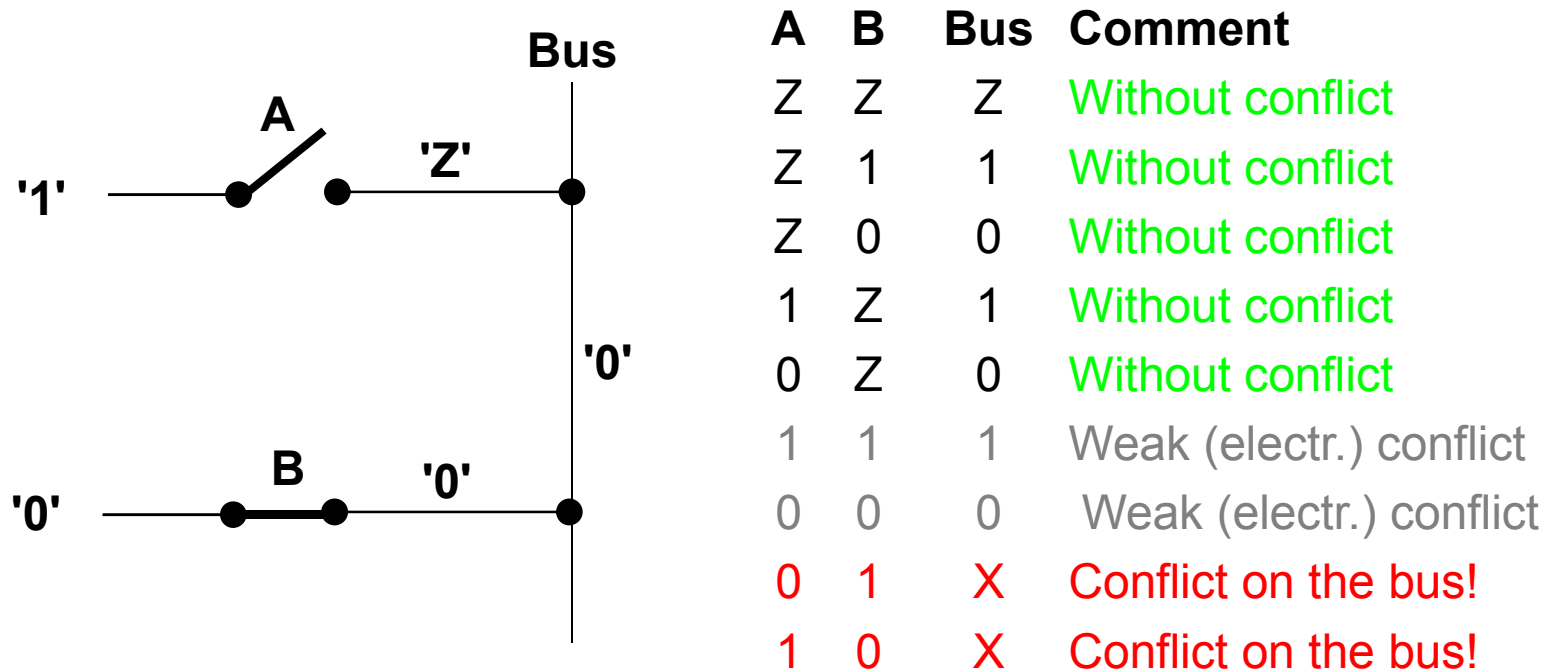**Conflict resolving – tri-state logic - maximum one signal can be in a low impedance state, others has to be in high impedance**


 
## Meaning of the STD\_LOGIC levels (cont.)

*Other STD\_LOGIC levels: '1', '0', 'H', 'L', 'W', 'Z'*



## Meaning of the STD\_LOGIC levels (cont.)

'\_'

- Any level
- Can be assigned to the output if the corresponding signal does not depend on input signals (synthesis results can be significantly improved, logic area can be reduced)
- Pay attention:  
'1' = '-' is FALSE



# User-defined types

## ⊕ *Enumerated types*

- Used to describe state machines
- Ex. :

```
TYPE state IS (wait, go, stop, error);
```

## ⊕ *Arrays*

- Ex. :

```
TYPE my_array IS ARRAY(0 TO 2, 0 TO 7);
```

- Based on this array, an object can be declared:


```
decl_objet: objet my_array;
```

*Declaration  
reference*


*Object name*

*Object type*

# VHDL design models

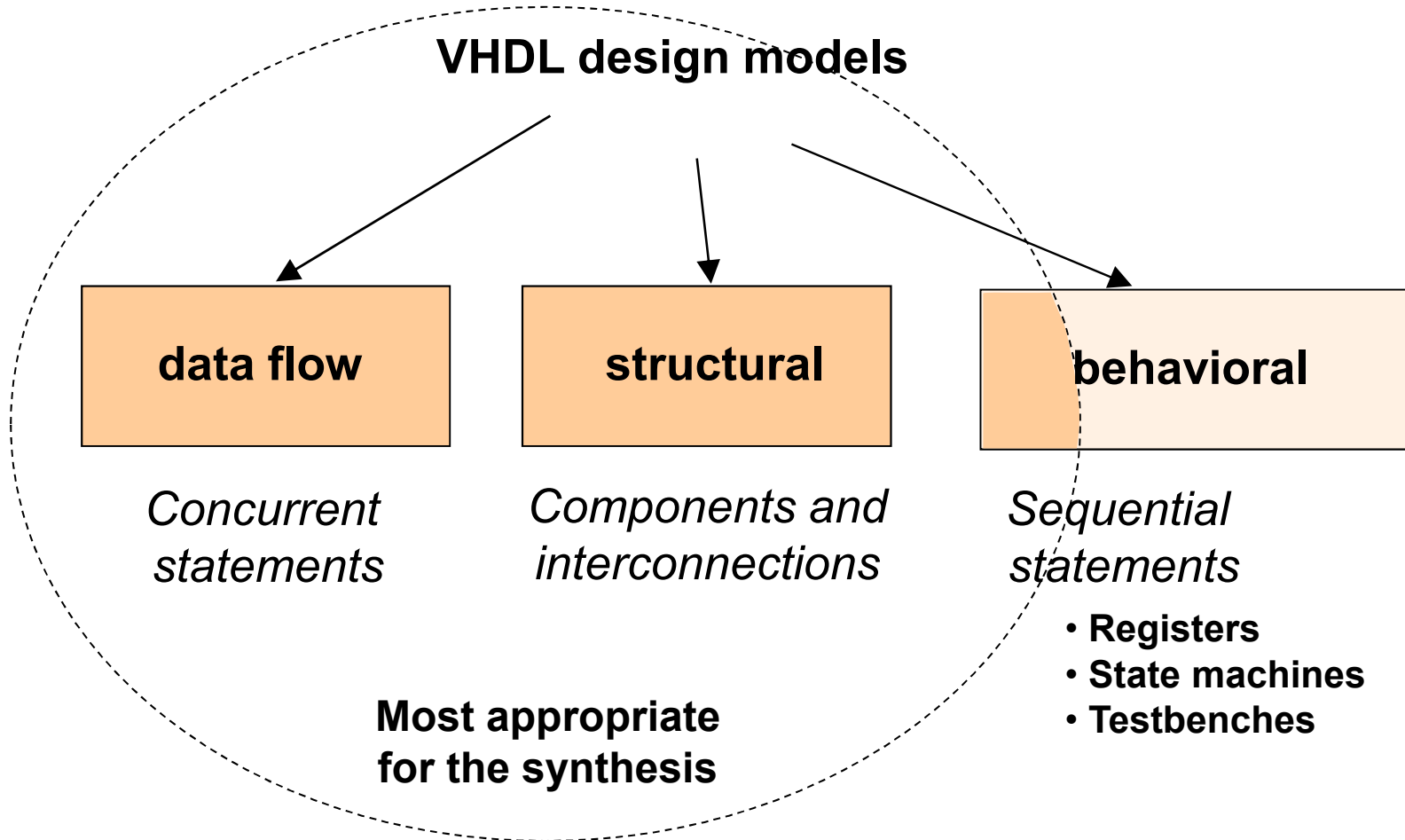


## Example : XOR3

 

```
ENTITY xor3 IS
  PORT (
    a      : IN STD_LOGIC;
    b      : IN STD_LOGIC;
    c      : IN STD_LOGIC;
    result : OUT STD_LOGIC
  );
END xor3;
```

# Dataflow architecture

 

*Architecture name*

*Entity name*

```
ARCHITECTURE xor3_dataflow OF xor3 IS
    SIGNAL u1_out: STD_LOGIC;
BEGIN
    u1_out <= a XOR b;
    result <= u1_out XOR c;
END xor3_dataflow;
```

*Internal signal declaration*

## Dataflow architecture (cont.)

- ⊕ Dataflow model describes relations between data inside the module.
- ⊕ It uses concurrent statements to realize the logic. Statements are evaluated simultaneously (in parallel), their order is therefore **not important!**
- ⊕ It is the most useful, if the logic can be represented using Boolean statements (combinatorial logic).

# Signals and constants

- ⊕ **Signal** – simple wire interconnection
- ⊕ **Two signal types**
  - Input/output signals (with direction)
  - Internal signals (without direction)
- ⊕ **Assignment of a value to a signal: operator <=**

Note: Internal signals can be eliminated by the compiler during optimization phase of the logic synthesis

Internal signals declaration examples:

```
SIGNAL dff, reset      : std_logic;  
SIGNAL internal_bus   : std_logic_vector(7 DOWNT0 0);  
SIGNAL zero, carry_out : bit;
```

List of signals separated by a comma

Signal types

## Signals and constants (cont.)

- ⊕ **Constant** – associates a fixed value to a signal
- ⊕ Constants use the same data types as signals (*bit*, *bit\_vector*, *std\_logic*, *std\_logic\_vector*)
- ⊕ Constants enhance readability of the code
- ⊕ Assignment of a value: operator :=

Constant declaration examples :

```
CONSTANT standby : bit_vector(1 DOWNTO 0) := "00";  
CONSTANT odd: std_logic_vector(2 DOWNTO 0) := "--1";  
CONSTANT hi_imp: std_logic_vector(0 TO 7) := "ZZZZZZZZ";
```

Another version of the last declaration:

```
CONSTANT hi_imp: std_logic_vector(0 TO 7)  
                := (OTHERS => 'Z');
```

Advantage : we do not need to know the number of vector elements

# Structural model of the architecture


```
ARCHITECTURE xor3_struct OF xor3 IS
  SIGNAL u1_out: STD_LOGIC;
  COMPONENT xor2
    PORT (
      i1 : IN STD_LOGIC;
      i2 : IN STD_LOGIC;
      y  : OUT STD_LOGIC
    );
  END COMPONENT;
BEGIN
  u1: xor2 PORT MAP (i1 => a,
                    i2 => b,
                    y  => u1_out);

  u2: xor2 PORT MAP (i1 => u1_out,
                    i2 => c,
                    Y  => result);
END xor3_struct;
```

*Internal signal declaration*

*Component declaration  
(it is defined elsewhere)*

*Component instantiation*

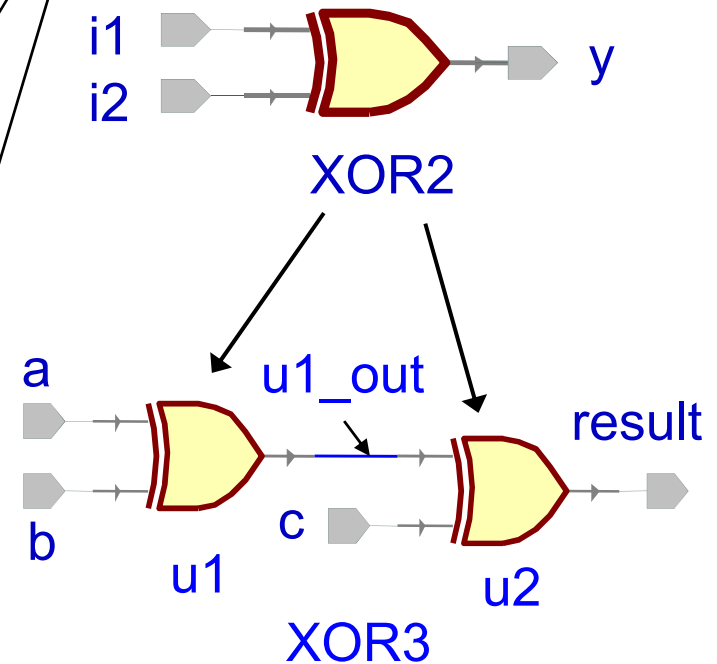





## Structural model of the architecture (cont.)

- ⊕ **It is easy to understand. It is close to schematics design: it uses simple blocks to create higher-level logic functions**
- ⊕ **Components can be interconnected in a hierarchical manner**
- ⊕ **In the structural model we can connect simple logic ports or complex (and abstract) components**
- ⊕ **The structural model of the architecture is useful if the blocks can be interconnected in a natural way**

# Component declaration and instantiation

- ⊕ Assignment of interconnections **by their names** - **recommended**

```
COMPONENT xor2 IS
  PORT (
    i1 : IN STD_LOGIC;
    i2 : IN STD_LOGIC;
    y  : OUT STD_LOGIC
  );
END COMPONENT;
```

← **Component declaration**  
(in the "declarations" part  
of the architecture)

```
u1: xor2 PORT MAP (i1 => a,
                  i2 => b,
                  y  => u1_out);
```

← **Component instantiation**  
(in the architecture body)

**Instantiation name**


**Component name**

## Component declaration and instantiation (cont.)

- ⊕ Assignment of connections **by their position** - **not recommended!**

```
COMPONENT xor2 IS
  PORT (
    i1 : IN STD_LOGIC;
    i2 : IN STD_LOGIC;
    y  : OUT STD_LOGIC
  );
END COMPONENT;

u1: xor2 PORT MAP (a, b, u1_out);
```

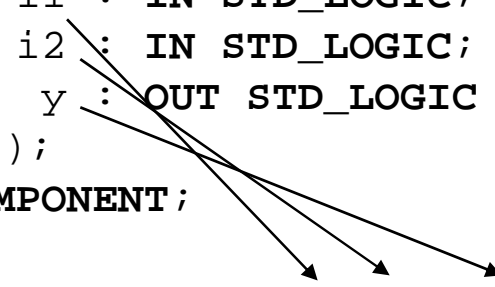

## Behavioral model of the architecture


```
ARCHITECTURE xor3_behav OF xor3 IS
BEGIN
  xor3_proc: PROCESS (a, b, c)
  BEGIN
    IF ((a XOR b XOR c) = '1') THEN
      result <= '1';
    ELSE
      result <= '0';
    END IF;
  END PROCESS xor3_proc;
END xor3_behav;
```

- ⊕ Behavioral model describes what happens at the output of the module (depending on input) without specification of the internal structure of the block (black-box approach)
- ⊕ It uses a VHDL structure called *Process*
- ⊕ **It is not recommended for combinatorial structures**

# Testbench

- ⊕ The *Testbench* applies the stimuli to the input of the component (Device Under Test – DUT) and (eventually) verifies the simulation results
- ⊕ The results can be observed in the simulator waveform window or they can be written to a file
- ⊕ Since the *Testbench* is written in VHDL, it is not restricted to the use of a specific simulation tool (portability notion)
- ⊕ The same *Testbench* can be easily adapted to test different implementations (e. g. different architectures) of the same project

## Testbench (cont.)

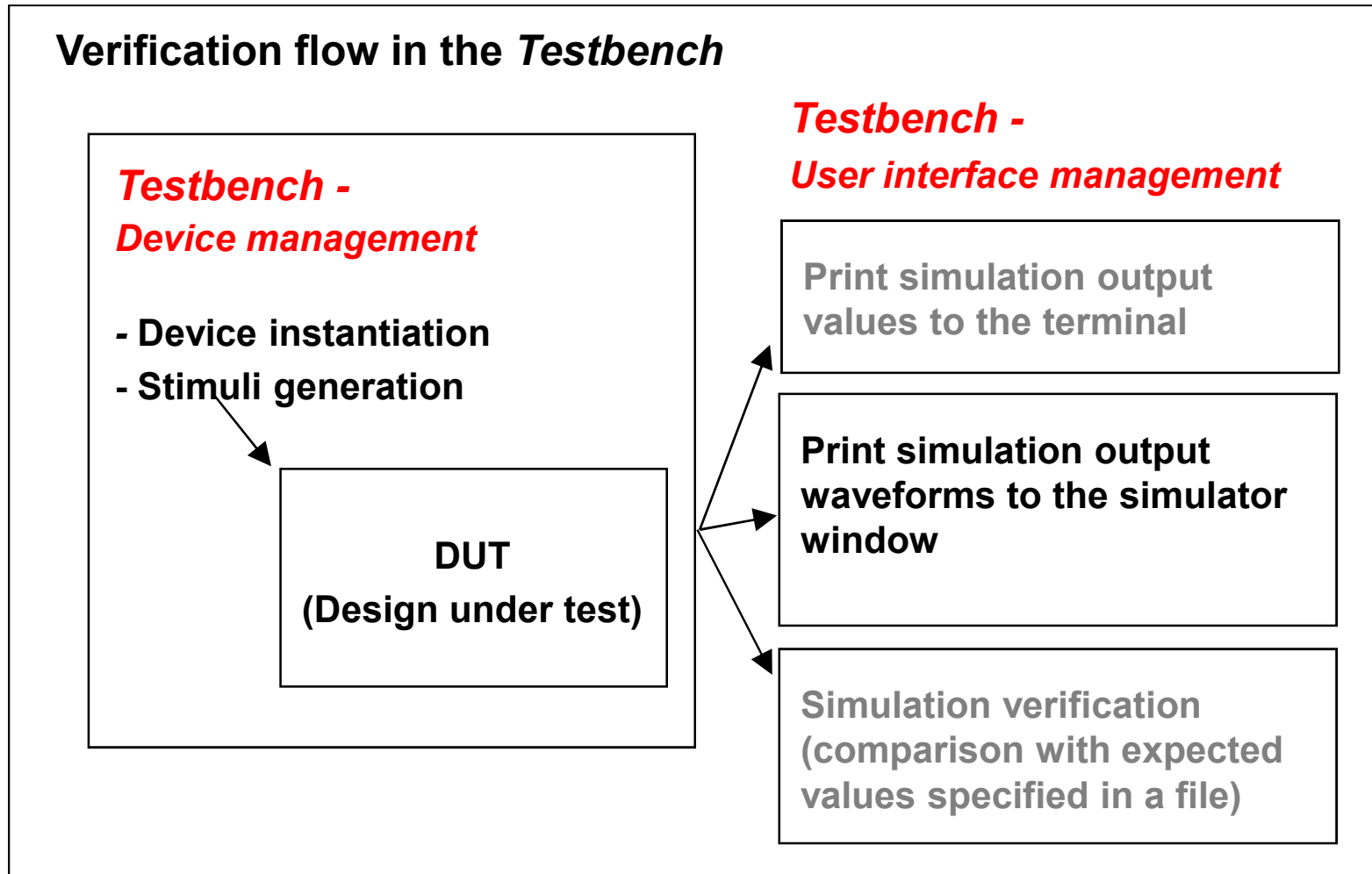

# Testbench – example

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tb_xor3 IS
END tb_xor3;

ARCHITECTURE structure OF tb_xor3 IS

    COMPONENT xor3
        PORT(
            a:      IN  std_logic;
            b:      IN  std_logic;
            c:      IN  std_logic;
            result: OUT std_logic
        );
    END COMPONENT;

    SIGNAL x1, x2, x3 : std_logic;
    SIGNAL y          : std_logic;

BEGIN

    u_xor3: xor3
        port map (
            a    => x1,
            b    => x2,
            c    => x3,
            result => y
        );
```

Testbench does not have ports!

DUT declaration

Declaration of internal signals

DUT instantiation

see next page ...

1



## Testbench – example (cont.)


```
stimuli: PROCESS                                ← Stimuli generation
BEGIN
  x1 <= '0';
  x2 <= '0';
  x3 <= '0';
  WAIT FOR 10 ns;
  x1 <= '1';
  x2 <= '0';
  x3 <= '0';
  WAIT FOR 10 ns;
  x1 <= '1';
  x2 <= '1';
  x3 <= '0';
  WAIT FOR 10 ns;
  x1 <= '1';
  x2 <= '1';
  x3 <= '1';
  WAIT FOR 10 ns;
  x1 <= 'X';
  x2 <= 'X';
  x3 <= '0';
  WAIT FOR 30 ns;
  x1 <= '1', '0' AFTER 10 ns, '1' AFTER 20 ns;
  x2 <= '1', '0' AFTER 20 ns;
  WAIT;                                          -- stop the process
END PROCESS stimuli;
END structure;
```

2



## Testbench – example (cont.)

Waveforms – simulation results:

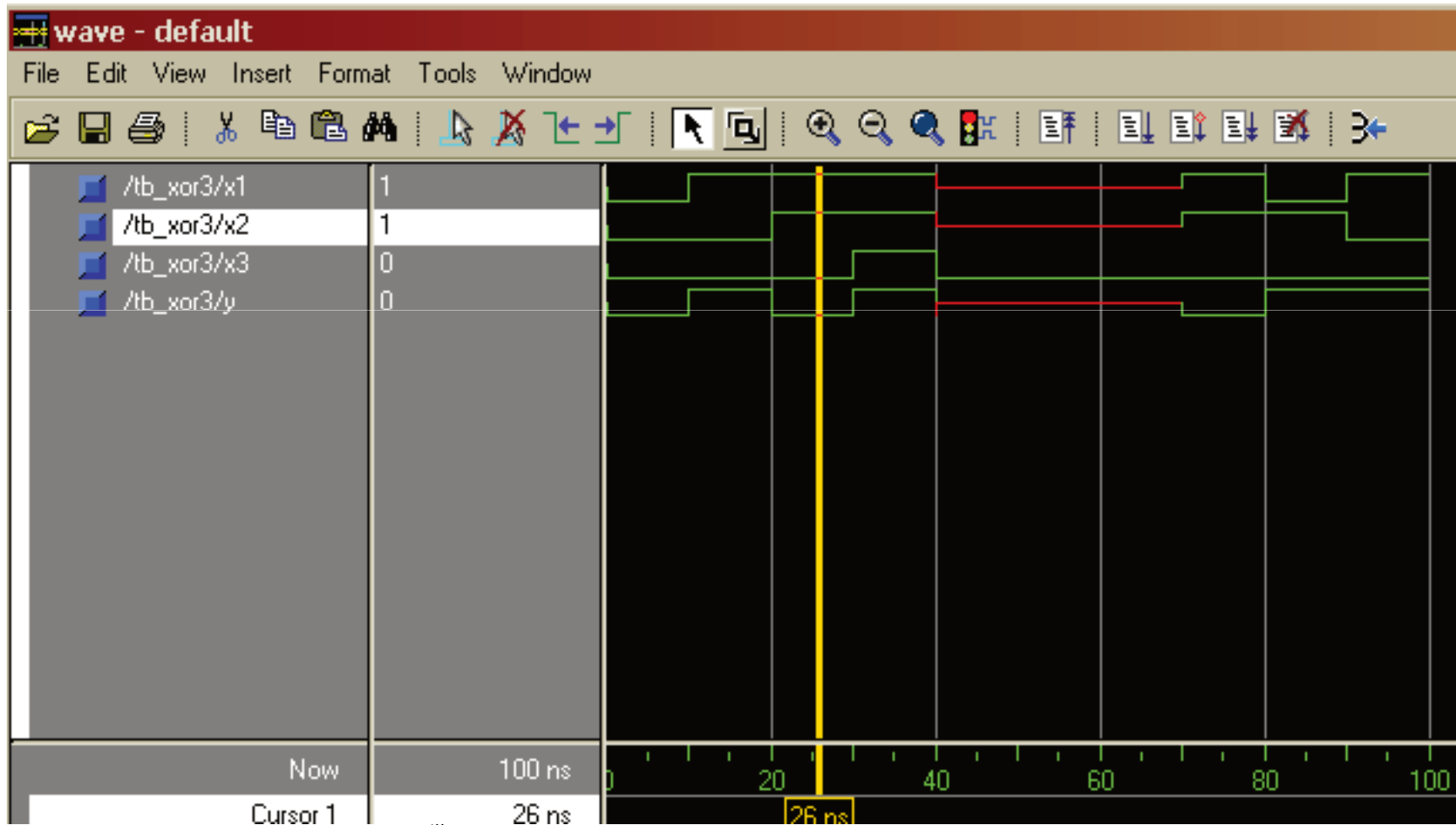



# Contents

- ⊕ ***Introduction***
- ⊕ ***VHDL basics***
- ⊕ ***Concurrent structures***
- ⊕ ***Applications of the concurrent structures***
  - decoders, parity checkers, multiplexers, arithmetic logic units, tri-state outputs, bi-directional inputs/outputs
- ⊕ ***Sequential structures***
- ⊕ ***Applications of the sequential structures***
  - latches, registers, counters
- ⊕ ***State machines***
- ⊕ ***Modularity and parameterization of modules***
- ⊕ ***Testbenches***

# Concurrent structures

## ⊕ **Concurrent instructions**

- **Unconditional** signal assignment
  - *signal* <= *expression (using signals)*;
- **Conditional** signal assignment
  - *signal* <= *expression1* **WHEN** *condition* **ELSE** *expression2*;
- **Selective** signal assignment
  - **WITH** *selector* **SELECT**  
*signal* <= *expression1* **WHEN** *selector\_value, ...*;

## ⊕ **Component instantiation**

## ⊕ **Multiple assignments/component instantiations**

- *label*: **FOR** *loop\_variable* **IN** *interval* **GENERATE**  
    *{concurrent instruction(s)}*  
    **END GENERATE** *label*;

## ⊕ **Conditional assignments/component instantiations**


- label*: **IF** *condition* **GENERATE**  
    *{concurrent instruction(s)}*  
    **END GENERATE** *label*;

## Concurrent instructions – example

```
ENTITY multiplexers IS
PORT (a, b, sel : IN bit;
      x, y, z   : OUT bit);
END multiplexers;


ARCHITECTURE rtl OF multiplexers IS
BEGIN
-- unconditional assignment
  x <= (a AND NOT sel) OR (b AND sel);

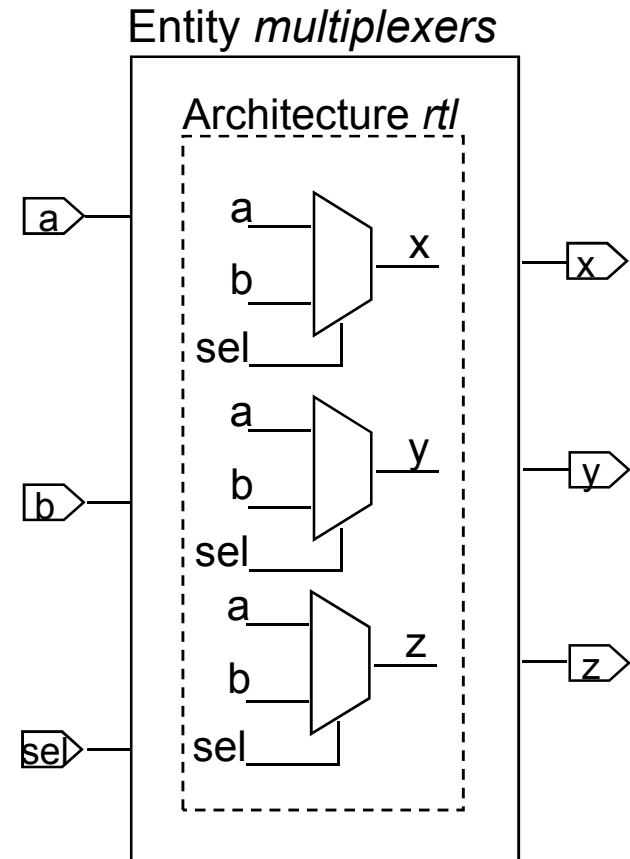-- conditional assignment
  y <= a WHEN sel='0' ELSE
      b;
-- selective assignment
  WITH sel SELECT
    z <= a  WHEN '0',
        b  WHEN '1',
        '0' WHEN OTHERS;
END rtl;
```


 
## Concurrent instructions – example (cont.)

- ⊕ Since **three instructions describe the same logic structure**, the architecture **rtl** will be implemented in the hardware in a following way - two redundant structures **will be deleted**



## Concurrent instructions (cont.)

### ⊕ **Conditional signal assignment**

- *signal* **<=** *expression (with signals)*;
- Example :

**a <= b AND c;**

(a takes the operation result value (b AND c))

### Logical operators

and	or	nand	nor	xor	not	xnor
-----	----	------	-----	-----	-----	------

### Relational operators

=	/=	<	<=	>	>=
---	----	---	----	---	----

### Priority of operators

not						
=	/=	<	<=	>	>=	
and	or	nand	nor	xor	xnor	

↓

## Concurrent instructions (cont.)

### ⊕ *Priority of operators – example:*

*Intended logic function:*

$$x = ab + cd$$

*Incorrect assignment:*

```
x <= a AND b OR c AND d;
```

*Equivalent to:*

```
x <= ((a AND b) OR c) AND d;
```

*Correct version:*

```
x <= (a AND b) OR (c AND d);
```

# Arithmetic operators

## *Additive operators*

- +** - addition
- - subtraction
- &** - concatenation of two vectors and **not a logical AND!**

## *Multiplicative operators - limited use in synthesis*

- \*** - multiplication
- /** - division
- mod** - modulo division
- rem** - remainder of the division

## *Other operators – shouldn't be used for the synthesis*

- \*\*** - squaring
- abs** - absolute value

**Additive operators + and – are defined only for integers and reals! For addition (subtraction) of bit (bit\_vector) and std\_logic (std\_logic\_vector) signals, it is necessary to use arithmetic library!!!**



## Concurrent instructions (cont.)

### ⊕ *Signal vectors and their concatenation*

```
SIGNAL a      : std_logic_vector(3 DOWNTO 0);  
SIGNAL b      : std_logic_vector(3 DOWNTO 0);  
SIGNAL c, d, e, f: std_logic_vector(7 DOWNTO 0);
```

```
a <= "0000";
```

```
b <= "1111";
```

```
c <= a & b;
```

```
d <= '0' & "0001111";
```

```
e <= '0' & '0' & '0' & '0' & '1' & '1' & '1' & '1';
```

```
f <= "0000" & (OTHERS => '1');
```

Character strings (numbers) are delimited by quotation marks

One character (number) is delimited by apostrophes

```
-- c <= "00001111"
```

```
-- d <= "00001111"
```

```
-- e <= "00001111"
```

```
-- f <= "00001111"
```

## VHDL operators - summary

Operator type	Operator name/symbol
Logical	and or nand nor xor xnor
Relational	= /= < <= > >=
Addition/subtraction	+ - &
Sign	+ -
Multiplication/division	* / mod rem
Miscellaneous	** abs not

**Operators in gray are not always supported!**


# Concurrent instructions

## ⊕ **Conditional assignment**

```
target_signal <= value1 WHEN condition1 ELSE  
value2 WHEN condition2 ELSE
```

...
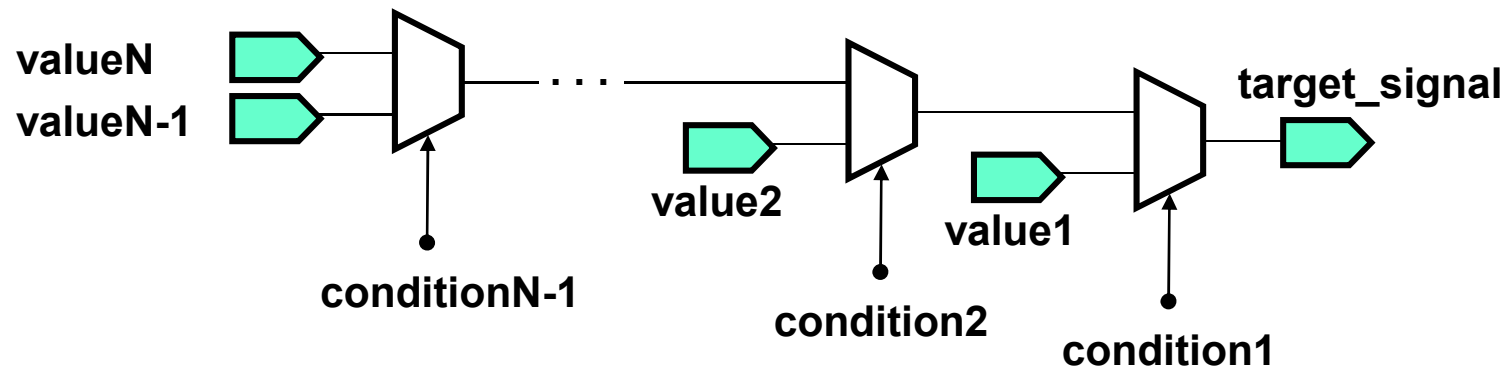
```
valueN-1 WHEN conditionN-1 ELSE  
valueN;
```




**Conclusion : caution – priority encoding!**

## Concurrent instructions (cont.)

```
-- conditional assignment  
y <= a WHEN sel1 = '1' ELSE  
  b WHEN sel2 = '1' ELSE  
  c;
```

Obtained logic

 

*Selection of signal a by  
the signal sel1 has  
**priority** before b and c!*

```
q = (sel1 AND a)  
  OR ((NOT sel1) AND sel2 AND b)  
  OR ((NOT sel1) AND (NOT sel2) AND c)
```


## Concurrent instructions (cont.)

### ⊕ **Selective assignment**

**WITH** *selector* **SELECT**

```
target_signal <= value1 WHEN selector_value,  
                value2 WHEN selector_value,  
                ...  
                valueN WHEN OTHERS;
```

Application example: **multiplexer**

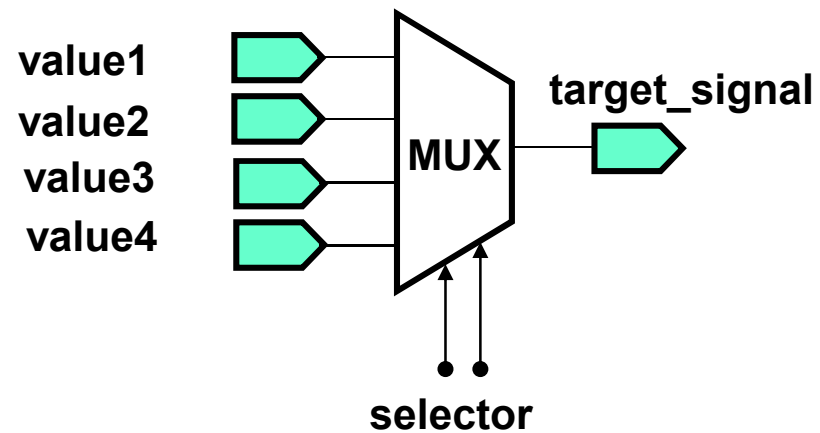

## Concurrent instructions (cont.)

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY multiplexer IS
PORT (a, b, c, d : IN std_logic;
      sel          : IN std_logic_vector(1 DOWNTO 0);
      y           : OUT std_logic);
END multiplexer;

ARCHITECTURE rtl OF multiplexer IS
BEGIN
-- selective assignment
  WITH sel SELECT
    y <= a  WHEN "00",
         b  WHEN "01",
         c  WHEN "10",
         d  WHEN OTHERS;
END rtl;
```

***Selection without priority!***

$$y = (a \text{ AND } (\text{NOT } sel(1)) \text{ AND } (\text{NOT } sel(0)))$$
$$\text{OR } (b \text{ AND } (\text{NOT } sel(1)) \text{ AND } sel(0))$$
$$\text{OR } (c \text{ AND } sel(1) \text{ AND } (\text{NOT } sel(0)))$$
$$\text{OR } (d \text{ AND } sel(1) \text{ AND } sel(0))$$

## Concurrent instructions (cont.)

### ⊕ **Structure *GENERATE* for concurrent instructions**

*label*: **FOR** *loop\_variable* **IN** *interval* **GENERATE**

*[declarations]*


**BEGIN**

*{concurrent assignment(s)}*

**END GENERATE** *label*;

Optional
 
### Application example: **parity generator**



## Concurrent instructions (cont.)

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY parity IS
PORT (par_in : IN std_logic_vector(7 DOWNTO 0);
      y      : OUT std_logic);
END parity;

ARCHITECTURE rtl OF parity IS
  SIGNAL par_int : std_logic_vector(7 DOWNTO 0);

BEGIN
  par_int(0) <= par_in(0);
  y <= par_int(7);
  Calc_parity:
  FOR i IN 1 TO 7 GENERATE
    par_int(i) <= par_in(i) XOR par_int(i-1);
  END GENERATE Calc_parity;
END rtl;
```

We can use the signal `par_int(7)` before a value is assigned to it (concurrent structure)

$y = \text{par\_in}(0) \text{ XOR } \text{par\_in}(1) \text{ XOR } \text{par\_in}(2) \text{ XOR } \text{par\_in}(3) \text{ XOR } \text{par\_in}(4) \text{ XOR } \text{par\_in}(5) \text{ XOR } \text{par\_in}(6) \text{ XOR } \text{par\_in}(7)$



# Contents

⊕ ***Introduction***

⊕ ***VHDL basics***

⊕ ***Concurrent structures***

⊕ ***Applications of the concurrent structures***

decoders, parity checkers, multiplexers, arithmetic logic units,  
comparators, tri-state outputs, bi-directional inputs/outputs

⊕ ***Sequential structures***

⊕ ***Applications of the sequential structures***

latches, registers, counters

⊕ ***State machines***

⊕ ***Modularity and parameterization of modules***

⊕ ***Testbenches***

# Applications of concurrent structures

## ⊕ *Implementation of combinatorial logic functions (CLF)*

### ⊕ *CLF - definition*

- *The output value of a CLF depends only on input signals values and (in contrast with a sequential logic function) it does not depend on the function internal state*
- *Exemple :*      $Y = f(A, B, C) = A + B + C$


### ⊕ *Combinatorial functional blocks*

#### *Application examples:*

- Simple combinatorial structures
- Multiplexers
- Parity generators
- Coders/decoders
- Comparators, arithmetic and logic unit
- Tri-state outputs
- Bi-directional inputs/outputs
- ...

## Applications of concurrent structures (cont.)

### ⊕ *Arithmetic and logic unit*

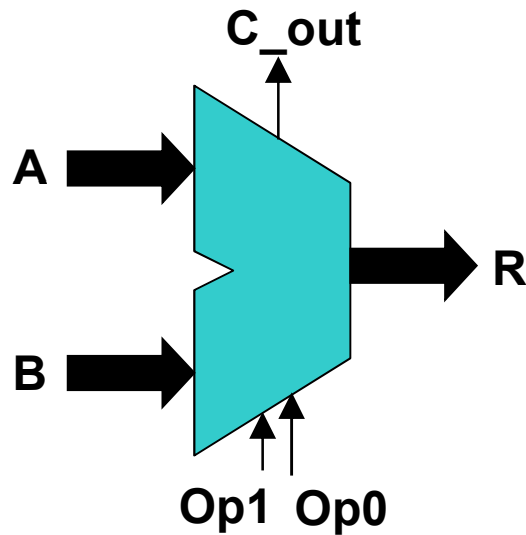

Op1	Op0	Operation
0	0	$R = A + B$
0	1	$R = A - B$
1	0	$R = A \text{ and } B$
1	1	$R = A \text{ or } B$

## Applications of concurrent structures (cont.)

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.ALL;

ENTITY alu IS
PORT (a, b      : IN std_logic_vector(7 DOWNTO 0);
      op1, op0  : IN std_logic;
      r        : OUT std_logic_vector(7 DOWNTO 0);
      c_out    : OUT std_logic);
END alu;

ARCHITECTURE rtl OF alu IS
    SIGNAL oper    : std_logic_vector(1 DOWNTO 0);
    SIGNAL int     : std_logic_vector(8 DOWNTO 0);

BEGIN
    oper    <= op1 & op0;  -- operation code
    c_out   <= int(8);
    r      <= int(7 DOWNTO 0);

    WITH oper SELECT
        int <= (('0' & a) + ('0' & b)) WHEN "00",
              (('0' & a) - ('0' & b)) WHEN "01",
              ('0' & (a AND b))      WHEN "10",
              ('0' & (a OR b))       WHEN OTHERS;


END rtl;
```

Packet necessary for arithmetic operations

Extension of *a* and *b* to 9 bits (the ninth bit will be the carry)

## Applications of concurrent structures (cont.)

### ⊕ *Tri-state outputs*

 


a	oe	y
0	0	Z
0	1	0
1	0	Z
1	1	1

```
-- conditional assignment  
y <= a WHEN oe = '1' ELSE  
    'Z';
```

**y has to be declared as a std\_logic  
and not as a bit!**


# Applications of concurrent structures (cont.)

## ⊕ *Open collector*

 


oe	y
0	Z
1	0
 
```
-- conditional assignment  
y <= '0' WHEN oe = '1' ELSE  
  'Z';
```



# Applications of concurrent structures (cont.)

## ⊕ *Bi-directional input/output*

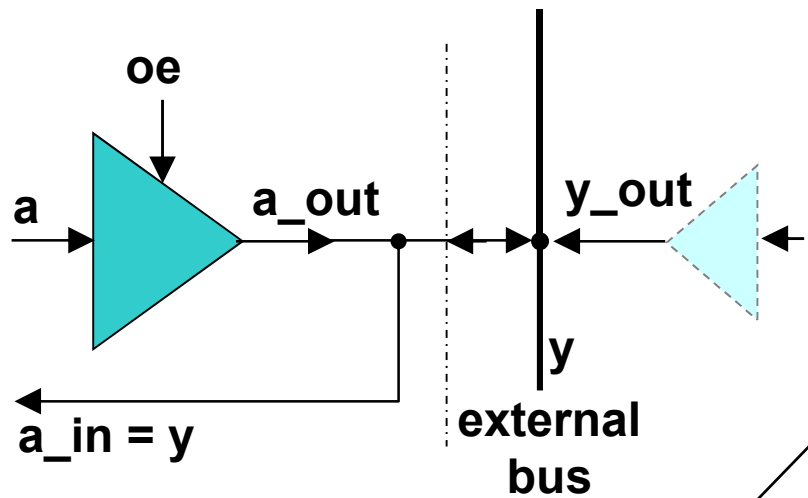

***a\_out* and *a\_in* can have different values**  
 (⇒ two signals are necessary for the simulation)

a	oe	a_out	y a_in	y_out
0	0	Z	Z	Z
0	1	0	→ 0	Z
1	0	Z	Z	Z
1	1	1	→ 1	Z
0	0	Z	0 ←	0
0	1	0	→ 0 ←	0
1	0	Z	0 ←	0
1	1	1	→ X ←	0
0	0	Z	1 ←	1
0	1	0	→ X ←	1
1	0	Z	1 ←	1
1	1	1	→ 1 ←	1

**Bus contentions!**

# Applications of concurrent structures (cont.)


```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY io_bidir IS
PORT (y      : INOUT std_logic;
      oe     : IN std_logic;
      a_log2bus : IN std_logic;
      a_bus2log : OUT std_logic);
END io_bidir;

ARCHITECTURE rtl OF io_bidir IS
BEGIN
  y <= a_log2bus WHEN oe = '1' ELSE
    'Z';
  a_bus2log <= y;
END rtl;

```

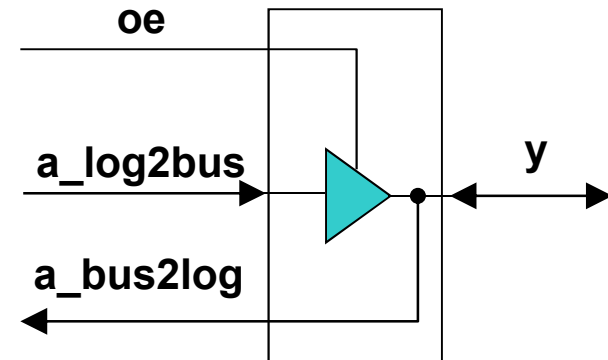


/tb_es_bidir/s_y_in	Z
/tb_es_bidir/s_oe	1
/tb_es_bidir/s_a_log2bus	1
/tb_es_bidir/s_a_bus2log	1
/tb_es_bidir/s_y	1

Stimulator

High impedance

Bus contentions

 



# Contents

- ⊕ ***Introduction***
- ⊕ ***VHDL basics***
- ⊕ ***Concurrent structures***
- ⊕ ***Applications of the concurrent structures***
  - decoders, parity checkers, multiplexers, arithmetic logic units, tri-state outputs, bi-directional inputs/outputs
- ⊕ ***Sequential structures***
- ⊕ ***Applications of the sequential structures***
  - latches, registers, counters
- ⊕ ***State machines***
- ⊕ ***Modularity and parameterization of modules***
- ⊕ ***Testbenches***

## Basic sequential structures

⊕ **Used only inside the *PROCESS*, *FUNCTION* and *PROCEDURE*!**

⊕ **Four basic structures:**

- **Unconditional** assignment of a signal or variable

*signal* <= *expression* (with signals);

*variable* := *expression* (with variables);

- **Conditional** structure

**IF** *condition* **THEN**

*{sequential instruction(s)}*

**/ELSIF** *condition* **THEN**

*{sequential instruction(s)}*

**/ELSE**

*{sequential instruction(s)}*

...

**END IF;**

Optional  
parts



## Basic sequential structures (cont.)

- **Selective** structure

**CASE** *selector* IS

**WHEN** *selector\_value1* =>

*{sequential instruction(s)}*

**WHEN** *selector\_value2* =>

*{sequential instruction(s)}*

**WHEN** *selector\_value3* =>

*{sequential instruction(s)}*

...

**WHEN OTHERS** =>

*{sequential instruction(s)}*


**END CASE;**

Optional, but  
recommended part

## Basic sequential structures (cont.)

- **Loop structures**
  - *Three basic types*
    - **Simple** loops (without iteration scheme)
    - **FOR** loops
    - **WHILE** loops
  - *Used mostly in **testbenches***

Syntax:

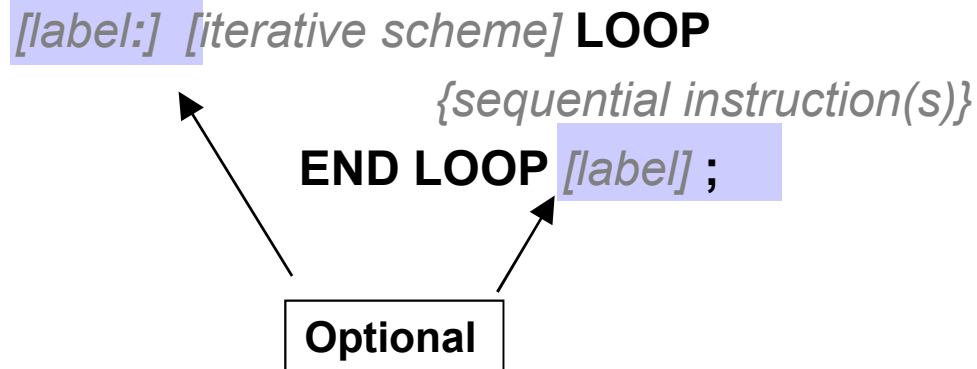

## Basic sequential structures (cont.)

- **Simple loop (infinite)**

**Syntax:**

`[label:] LOOP`

*{sequential instruction(s)}*

`END LOOP [label] ;`

Optional

- **Exit from the loop by**

`EXIT [WHEN condition] ;` unconditional exit from the loop

`NEXT [WHEN condition] ;` jump to the next iteration

`RETURN ... ;` in a function

## Basic sequential structures (cont.)

- **Loop FOR**

```
[label :] FOR loop_variable IN interval LOOP  
    {sequential instruction(s)}  
END LOOP [label] ;
```

Optional

- Loop variable does not need to be declared!

- **Loop WHILE**


```
[label :] WHILE condition LOOP  
    {sequential instruction(s)}  
END LOOP [label] ;
```

Optional

- Loops while the condition is true.
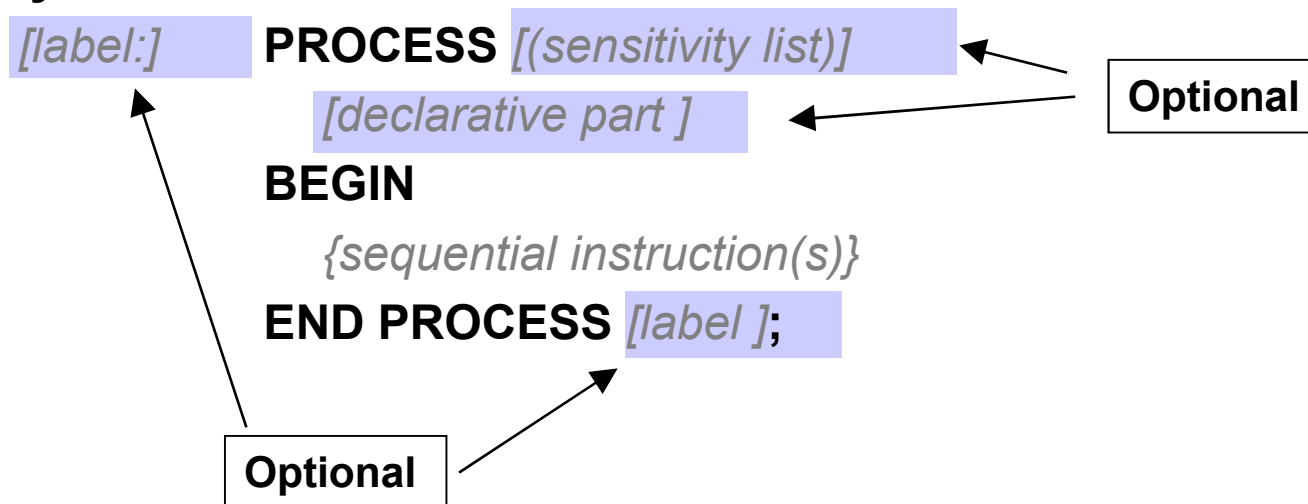
# PROCESS

- ⊕ Series of VHDL instructions with a **sequential behavior**
- ⊕ **Instruction order - important!**
- ⊕ Three phases of the PROCESS:
  - Standby, Activation, Execution
- ⊕ **Syntax:**





## Activation of the PROCESS and updating of the signal values

### ⊕ Two activation possibilities:

- **At any change of activating signals** given in the sensitivity list (several activating signals can be used), this type of activation is used mostly to realize:
  - latches,
  - registers
  - state machines
- **Following a waiting period** limited by an event (WAIT UNTIL) or by a period length (time) specification - WAIT FOR (only one of these parameters is allowed), this activation type is used mostly in:
  - testbenches

### ⊕ The signals are **evaluated during** the PROCESS, but **updated at the end** of the PROCESS



## Two PROCESS interpretations


- **Compiler infers a combinatorial structure**

- Sensitive to all signals used in the combinatorial logic

 **Example**

```
PROCESS(a, b, sel)
```

*sensitivity list contains all signals referenced in the process*




- **Compiler infers a sequential structure**

- Sensitive to the clock signal and to asynchr. control signals (reset, preset)

 **Example**


```
PROCESS(clr, clk)
```

*sensitivity list does not contain input D, only clock and asynchronous control signals*


 
## Implementation of several PROCESSES

- ⊕ An architecture can contain **several PROCESSES**
- ⊕ They are **executed in parallel**, because they are situated in the concurrent part of the architecture
- ⊕ Inside the PROCESS, the instructions are **executed sequentially**, the PROCESS is a sequential structure
- ⊕ Reduction of the number of processes **increases readability**



## Example of two equivalent structures

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY simp IS
PORT(a, b : IN std_logic;
      x : OUT std_logic);
END simp;
ARCHITECTURE exam OF simp IS
    SIGNAL c : std_logic;

BEGIN

    c <= a AND b;
    x <= c;

END exam;
```

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY simp_prc IS
PORT(a,b : IN std_logic;
      x : OUT std_logic);
END simp_prc;
ARCHITECTURE exam OF simp_prc IS
    SIGNAL c : STD_LOGIC;

BEGIN
    process1: PROCESS(a, b)
        BEGIN
            c <= a and b;
        END PROCESS process1;
    process2: PROCESS(c)
        BEGIN
            x <= c;
        END PROCESS process2;
END exam;
```

**c and x are updated in parallel  
at the end of the PROCESS**

# Two structures that give the same result after the synthesis, but not in the functional simulation


```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY simp IS
PORT(a, b : IN std_logic;
      x : OUT std_logic);
END simp;
ARCHITECTURE exam OF simp IS
SIGNAL c : std_logic;
BEGIN
  c <= a AND b;
  x <= c;
END exam;

```

 **A**

*simulation before and after the synthesis of A*



*post-synthesis simulation of B*


```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY simp_prc IS
PORT(a,b : IN std_logic;
      x : OUT std_logic);
END simp_prc;
ARCHITECTURE exam OF simp_prc IS
SIGNAL c : STD_LOGIC;
BEGIN
  PROCESS(a, b)
  BEGIN
    c <= a and b;
    x <= c;
  END PROCESS;
END exam;

```

**B**

*functional simulation of B*

 



## Two structures that give the same result after the synthesis, but not in the functional simulation (cont.)

### ⊕ Conclusions :

- **Do not use PROCESS to implement combinatorial logic, if not, caution!**
- **Use the PROCESS to implement sequential logic (containing storage elements)**
  - Latches
  - Registers
  - State machines
- **Use the PROCESS freely to realize testbenches**

# Contents

- ⊕ ***Introduction***
- ⊕ ***VHDL basics***
- ⊕ ***Concurrent structures***
- ⊕ ***Applications of the concurrent structures***
  - decoders, parity checkers, multiplexers, arithmetic logic units, tri-state outputs, bi-directional inputs/outputs
- ⊕ ***Sequential structures***
- ⊕ ***Applications of the sequential structures***
  - latches, registers, counters
- ⊕ ***State machines***
- ⊕ ***Modularity and parameterization of modules***
- ⊕ ***Testbenches***

# Sequential logic functions

## ⊕ *Sequential logic function - definition*

- *The next output value of the function depends on the current inputs AND on the current state – this needs implicitly the use of a memory element*

## ⊕ *Two main types*

- *Asynchronous logic – state can change any time*
- *Synchronous logic – state can change only in pre-defined time intervals – rising or falling edge of clock signals*

## ⊕ *Basis sequential functions*


- *Asynchronous flip-flops – RS, D latch*
- *Synchronous flip-flops - D, T, RS, JK*
- *Synchronous and asynchronous counters*
- *Registers and shift registers*
- *State machines*



# Basic sequential blocks
 
## Asynchronous flip-flops

- ⊕ **Flip-flop** – bi-stable circuit, able to store one bit
  - Storage element is often realized by a loop (the output of the function comes back to the input)
- ⊕ **Asynchronous RS flip-flop** – flip-flop serving as a building element for all other flip-flops (**S = Set**, **R = Reset**)
- ⊕ **RS flip-flop with NAND gates**



Truth table

S	R	Q <sup>+</sup>	nQ <sup>+</sup>	Next state
0	0	$\bar{Q}$	$\bar{nQ}$	Previous state
0	1	0	1	Reset
1	0	1	0	Set
1	1	Ambiguous		Forbidden




# Basic sequential blocks

## Asynchronous flip-flops (cont.)
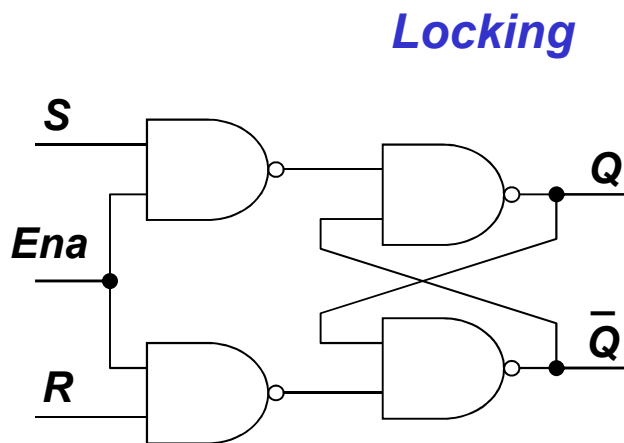
### ⊕ *RS flip-flop with locking*

*If input  $Ena = 0$ , the flip-flop is locked*





*Truth table*

Ena	S	R	$Q^+$	$nQ^+$
0	0	0	$\bar{Q}$	$\bar{nQ}$
0	0	1	$\bar{Q}$	$\bar{nQ}$
0	1	0	$\bar{Q}$	$\bar{nQ}$
0	1	1	$\bar{Q}$	$\bar{nQ}$
1	0	0	$\bar{Q}$	$\bar{nQ}$
1	0	1	0	1
1	1	0	1	0
1	1	1	<b>Ambiguous</b>	

# Basic sequential blocks

## Asynchronous flip-flops (cont.)
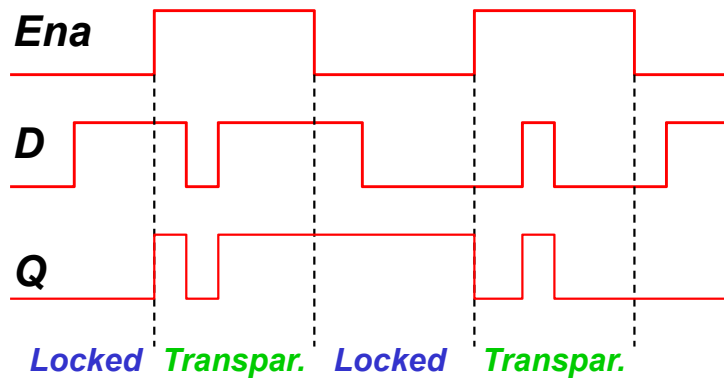 
### ⊕ *D flip-flop with locking – D Latch*



*Truth table*

Ena	D	Q <sup>+</sup>	nQ <sup>+</sup>
0	0	-Q	-nQ
0	1	-Q	-nQ
1	0	0	1
1	1	1	0

# Basic sequential blocks

## Asynchronous flip-flops (cont.)

### ⊕ *D latch using a data flow architecture*

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY d_latch IS
PORT ( d      : IN std_logic;
      ena     : IN std_logic;
      q       : OUT std_logic
      );
END d_latch;

ARCHITECTURE data_flow OF d_latch IS
    SIGNAL n_s, n_r      : std_logic;
    SIGNAL q_int, n_q_int : std_logic;
BEGIN
    n_s      <= NOT (d AND ena);
    n_r      <= NOT ((NOT d) AND ena);
    --
    n_q_int <= NOT (q_int AND n_r);
    q_int   <= NOT (n_q_int AND n_s);
    --
    q       <= q_int;
END data_flow;
```

**Data flow  
architecture based  
on the previous  
circuit diagram**

# Basic sequential blocks

## Asynchronous flip-flops (cont.)

- ⊕ *D latch using a behavioral description – VERY easy to read and understand its behavior*

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY d_latch IS
PORT ( d    : IN std_logic;
      ena   : IN std_logic;
      q     : OUT std_logic
      );
END d_latch;

ARCHITECTURE behavior OF d_latch IS
BEGIN
  PROCESS (ena, d)
  BEGIN
    IF ena = '1' THEN
      q <= d;
    END IF;
  END PROCESS;
END behavior;
```

Sensitivity list contains both inputs

If ena = '0'? => **Implicit memory!**

# Basic sequential blocks

## Synchronous flip-flops


⊕ **Synchronous flip-flop** – bi-stable circuit, changing its state only on the rising (or falling) edge of a clock signal

⊕ **Basic types**

- **D flip-flop**
- **JK flip-flop**
- **T flip-flop**
- **RS flip-flop**

⊕ Besides synchronous inputs, one or two **asynchronous control inputs** can be employed

 
- **Asynchronous reset**
- **Asynchronous preset**




# Basic sequential blocks
 
## Synchronous flip-flops (cont.)

- ⊕ **Synchronous D flip-flop** – the value present at the D input during the rising (or falling) edge of the clock signal is stored in the flip-flop until the next rising (or falling)



*Sensitivity on the rising edge*

 

*Truth table*


clk	D	Q <sup>+</sup>	nQ <sup>+</sup>
0	x	$\bar{Q}$	$\bar{n}Q$
1	x	$\bar{Q}$	$\bar{n}Q$
↓	x	$\bar{Q}$	$\bar{n}Q$
↑	0	0	1
↑	1	1	0

## D Flip - Flop using expression `clk = '1'`

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY dff IS
PORT ( d : IN std_logic;
      clk : IN std_logic;
      q : OUT std_logic
      );
END dff;

 ARCHITECTURE behav OF dff IS
BEGIN
PROCESS (clk)
BEGIN
  IF clk = '1' THEN
    q <= d;
  END IF;
END PROCESS;
END behav;
```



*sensitivity list contains activating signal*

*clk = '1' means activation on the rising edge (?)  
- NOT for std\_logic*

***Version to be avoided!***




# D flip-flop implementation using expression Wait

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY wait_dff IS
PORT ( d, clk : IN std_logic;
      q : OUT std_logic
      );
END wait_dff;

 ARCHITECTURE behav OF wait_dff IS
BEGIN
  PROCESS
  BEGIN
    WAIT UNTIL clk = '1';
    q <= d;
  END PROCESS;
END behav;
```



**Note: with WAIT, the sensitivity list cannot be used!**  
**Asynchronous reset is impossible!**


**WAIT UNTIL – replaces the sensitivity list**


 
## D flip-flop implementation – clk'event and clk = '1'

```
ENTITY dff_a IS
PORT ( d : IN bit;
      clk : IN bit;
      q : OUT bit
      );
END dff_a;

ARCHITECTURE behav OF dff_a IS
BEGIN
PROCESS (clk)
BEGIN
  IF clk'event and clk = '1' THEN
    q <= d;
  END IF;
END PROCESS;
END behav;
```



**clk'event and clk :**

- **clk** – clock signal
- **event** – VHDL attribute
- **clk = '1'** – PROCESS activation on the rising edge of the clock signal


**Recommended version for a bit-type signal! IEEE library is not needed.**

## D flip-flop implementation – rising\_edge

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY dff_b IS
PORT ( d : IN std_logic;
      clk : IN std_logic;
      q : OUT std_logic
      );
END dff_b;

 ARCHITECTURE behav OF dff_b IS
BEGIN
  PROCESS(clk)
  BEGIN
    IF rising_edge(clk) THEN
      q <= d;
    END IF;
  END PROCESS;
END behav;
```



### *rising\_edge :*

- VHDL function defined in the packet `std_logic_1164`
- specifies that the signal **has to pass** from 0 to 1
- transition from X, Z to 1 is not taken into account


**Recommended version for `std_logic`-type signals, but it needs the packet `std_logic_1164`!**

## D flip-flop with asynchronous reset

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
USE ieee.std_logic_unsigned.ALL;
```

```
ENTITY dff_clr IS  
PORT ( clr : IN std_logic;  
      d, clk : IN std_logic;  
      q : OUT std_logic  
    );  
END dff_clr;
```
 
```
ARCHITECTURE behav OF dff_clr IS  
BEGIN  
  PROCESS(clk, clrn)  
  BEGIN  
    IF clrn = '0' THEN  
      q <= '0';  
    ELSIF rising_edge(clk) THEN  
      q <= d;  
    END IF;  
  END PROCESS;  
END behav;
```




- Note: the condition concerning reset is before the condition **rising\_edge**, it has **PRIORITY**
- **clr = '0'** does not depend on the clock - it implements an asynchronous reset

# Basic sequential blocks

 
## Synchronous flip-flops (cont.)

- ⊕ **JK synchronous flip-flop** – behaviour similar to that of the RS flip-flop (J input works as S and K input as R), except for the case when J and K were equal to one, in this case the output is inverted



sensitivity on the rising edge

sensitivity on the falling edge

 

Truth table

clk	J	K	Q <sup>+</sup>	nQ <sup>+</sup>	Next state
0	x	x	$\bar{Q}$	$\bar{nQ}$	Previous state
1	x	x	$\bar{Q}$	$\bar{nQ}$	Previous state
↓	x	x	$\bar{Q}$	$\bar{nQ}$	Previous state
↑	0	0	$\bar{Q}$	$\bar{nQ}$	Previous state
↑	1	0	1	0	Set
↑	0	1	0	1	Reset
↑	1	1	$\bar{nQ}$	$\bar{Q}$	Inversion

# Basic sequential blocks

## Synchronous flip-flops (cont.)

### ⊕ Synchronous JK flip-flop - behavioral description

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY jk_ff IS
PORT ( j, k, clk : IN std_logic;
      q          : OUT std_logic
      );
END jk_ff;
ARCHITECTURE behavior OF jk_ff IS
    SIGNAL sel    : std_logic_vector(1 DOWNTO 0);
    SIGNAL q_int  : std_logic;
BEGIN
    sel <= j & k;
    PROCESS (clk)
    BEGIN
        IF rising_edge(clk) THEN
            CASE sel IS
                WHEN "10" => q_int <= '1';
                WHEN "01" => q_int <= '0';
                WHEN "11" => q_int <= NOT q_int;
                WHEN OTHERS => q_int <= q_int;
            END CASE;
        END IF;
    END PROCESS;
    q <= q_int;
END behavior;
```

set

reset

inversion

storing


## How many registers ?

```
ENTITY reg1 IS
    PORT ( d      : IN bit;
          clk    : IN bit;
          q      : OUT bit);
END reg1;

ARCHITECTURE reg1_a OF reg1 IS
    SIGNAL a, b : BIT;
BEGIN
    PROCESS (clk)
    BEGIN
        IF clk'event and clk = '1' THEN
            a <= d;
            b <= a;
            q <= b;
        END IF;
    END PROCESS;
END reg1_a;
```
 
## How many registers ... (solution)

- ⊕ **Signal assignment inside the structure IF-THEN (which tests the clock signal) infers registers**





## How many registers?

```
ENTITY reg1 IS
    PORT ( d      : IN bit;
          clk    : IN bit;
          q      : OUT bit);
END reg1;


ARCHITECTURE reg1_a OF reg1 IS
    SIGNAL a, b : BIT;
BEGIN
    PROCESS (clk)
    BEGIN
        IF clk'event and clk = '1' THEN
            a <= d;
            b <= a;
        END IF;
    END PROCESS;
    q <= b;
END reg1_a;
```

*Signal assignment  
is displaced*


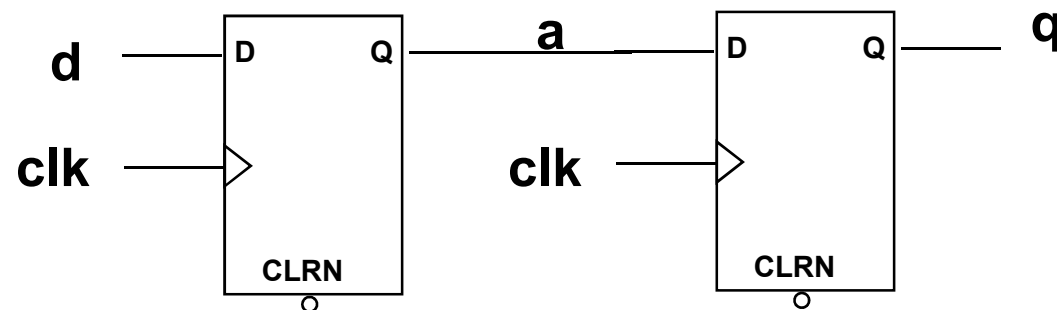
## How many registers ... (solution)

- ✦ Assignment of *b* to *q* does not depend on the rising edge of the clock signal, because it is not inside the structure IF-THEN that awaits the rising edge of the clock signal



# How many registers?

```
ENTITY reg1 IS
  PORT ( d      : IN bit;
         clk    : IN bit;
         q      : OUT bit);
END reg1;


ARCHITECTURE reg1_a OF reg1 IS
BEGIN
  PROCESS (clk)
    VARIABLE a, b : BIT;
  BEGIN
    IF clk'event and clk = '1' THEN
      a := d;
      b := a;
      q <= b;
    END IF;
  END PROCESS;
END reg1_a;
```

*Declaration of variables*

*Signals modified to variables*
 
## How many registers ... (solution)

- ⊕ **Variable** assignment is **updated instantly**
- ⊕ **Signal** assignment is **updated on the rising edge** of the clock signal
- ⊕ **Conclusion** : only one flip-flop will be implemented!



## Variable assignment in the sequential logic


- ⊕ The variables represent **temporary storage in the sequential structures** – PROCESS, FUNCION, PROCEDURE – they are not visible outside these structures
- ⊕ Variable assignment inside the structure IF-THEN that test the clock signal phase, **will not infer registers**
- ⊕ Variable assignment represent temporary storage of some value **without intention to be materialized**
- ⊕ Variable assignment can be used in expressions to update immediately their value, the variable can then be **assigned to a signal**

## Up/down counter using a variable

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.ALL;

ENTITY count_a IS
PORT (clk, rst, updn : IN std_logic;
      q : OUT std_logic_vector(15 DOWNTO 0));
END count_a;

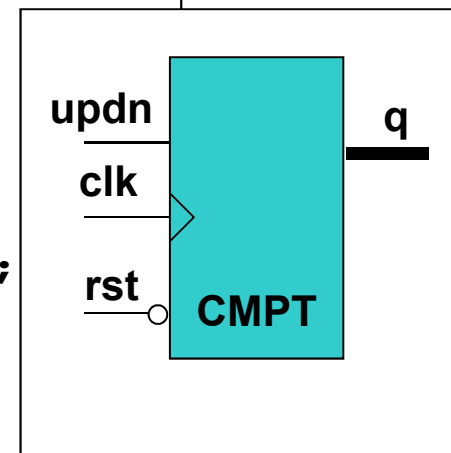ARCHITECTURE logic OF count_a IS
BEGIN
  PROCESS(rst, clk)
    VARIABLE tmp_q : std_logic_vector(15 DOWNTO 0);
  BEGIN
    IF rst = '0' THEN
      q <= (OTHERS => '0');
    ELSIF rising_edge(clk) THEN
      IF updn = '1' THEN
        tmp_q := tmp_q + 1;
      ELSE
        tmp_q := tmp_q - 1;
      END IF;
      q <= tmp_q;
    END IF;
  END PROCESS;
END logic;
```



*Arithmetic expressions assigned to a variable*

*A variable assigned to a signal inside the structure IF-THEN that awaits the clock signal will infer registers*

# Up/down counter using a signal


```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.ALL;

ENTITY count_a IS
PORT (clk, rst, updn : IN std_logic;
      q : OUT std_logic_vector(15 DOWNT0 0));
END count_a;

ARCHITECTURE logic OF count_a IS
  SIGNAL int_q : std_logic_vector(15 DOWNT0 0);
BEGIN
  PROCESS(rst, clk)
  BEGIN
    IF rst = '0' THEN
      int_q <= (OTHERS => '0');
    ELSIF rising_edge(clk) THEN
      IF updn = '1' THEN
        int_q <= int_q + 1;
      ELSE
        int_q <= int_q - 1;
      END IF;
    END IF;
  END PROCESS;
  q <= int_q;
END logic;

```

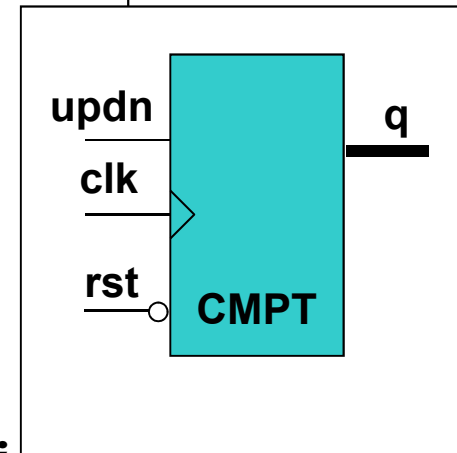

*Internal signal declaration  
(an output signal cannot be  
referenced in the right-side  
expression)*

*The signal value is stored until the  
next rising edge of the clock signal*


*Output signal assignment*

# Loadable counter

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.ALL;

ENTITY load_cnt IS
PORT (clk, rst, load : IN std_logic;
      d : IN std_logic_vector(15 DOWNTO 0);
      q : OUT std_logic_vector(15 DOWNTO 0));
END load_cnt;
```

```
ARCHITECTURE logic OF load_cnt IS
    SIGNAL int_q : std_logic_vector(15 DOWNTO 0);
BEGIN
    PROCESS(rst, clk)
    BEGIN
        IF rst = '0' THEN
            int_q <= (OTHERS => '0');
        ELSIF rising_edge(clk) THEN
            IF load = '1' THEN
                int_q <= d;
            ELSE
                int_q <= int_q + 1;
            END IF;
        END IF;
    END PROCESS;
    q <= int_q;
END logic;
```

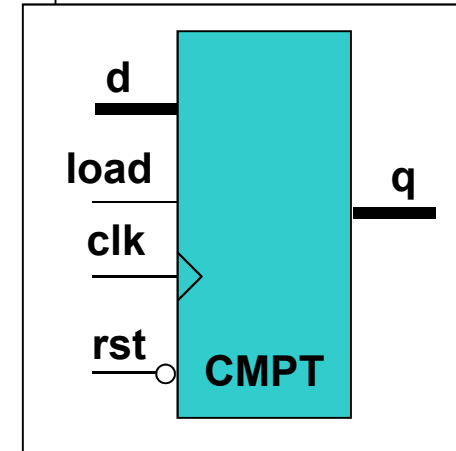

*Asynchronous branch (reset) is situated before the structure sensitive to the clock signal*

*Synchronous branch:  
- loading  
- incrementing*




## Loadable counter with counter enable

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.ALL;

ENTITY load_cnt IS
PORT (clk, rst, load : IN std_logic;
      d : IN std_logic_vector(15 DOWNTO 0);
      q : OUT std_logic_vector(15 DOWNTO 0));
END load_cnt;

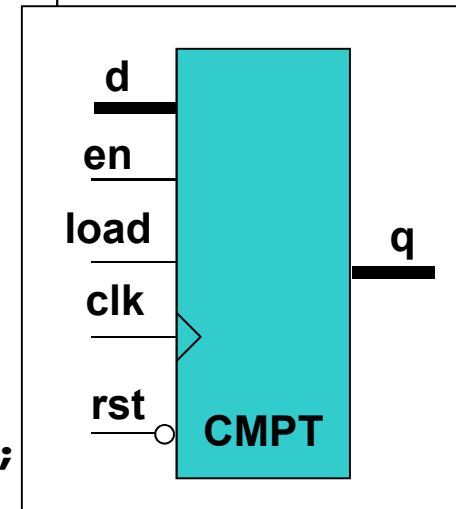ARCHITECTURE logic OF load_cnt IS
  SIGNAL int_q : std_logic_vector(15 DOWNTO 0);
BEGIN
  PROCESS(rst, clk)
  BEGIN
    IF rst = '0' THEN
      int_q <= (OTHERS => '0');
    ELSIF rising_edge(clk) THEN
      IF load = '1' THEN int_q <= d;
      ELSIF en = '1' THEN int_q <= int_q + 1;
      END IF;
    END IF;
  END PROCESS;
  q <= int_q;
END logic;
```



*Missing ELSE causes an implicit storage of the signal int\_q*



# Implicit storage in conditional structures


```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;

ENTITY implic_mem IS
PORT ( a, b      : IN std_logic;
      x1, y1, x2, y2 : OUT std_logic
      );
END implic_mem;

ARCHITECTURE behav OF implic_mem IS
BEGIN
  x1 <= a WHEN b = '1';
  y1 <= a WHEN b = '1' ELSE '0';
  PROCESS(b)
  BEGIN
    IF b = '1' THEN
      x2 <= a;
    END IF;
    IF b = '1' THEN
      y2 <= a;
    ELSE
      y2 <= '0';
    END IF;
  END PROCESS;
END behav;
```

The branch ELSE is omitted –  
implicit storage!

**Attention to omissions!**

 

## Concurrent and sequential structures - summary

Concurrent structures	Sequential structures
<b>Unconditional assignment</b> ... <= ...	<b>Unconditional assignment</b> ... <= ...
<b>Conditional assignment</b> ... <= ... <b>WHEN ... ELSE ...</b>	<b>Conditional structure</b> <b>IF ... THEN ... ELSE ... END IF</b>
<b>Selective assignment</b> <b>WITH ... SELECT</b> ... <= ... <b>WHEN ...</b>	<b>Selective structure</b> <b>CASE ... IS</b> <b>WHEN ... =&gt; ...</b> <b>END CASE</b>
<b>Structures GENERATE</b> <b>FOR ... GENERATE ...</b> <b>END GENERATE</b>	<b>Structures LOOP</b> <b>FOR ... LOOP ...</b> <b>END LOOP</b>

# Contents


- ⊕ ***Introduction***
- ⊕ ***VHDL basics***
- ⊕ ***Concurrent structures***
- ⊕ ***Applications of the concurrent structures***
  - decoders, parity checkers, multiplexers, arithmetic logic units, comparators, tri-state outputs, bi-directional inputs/outputs
- ⊕ ***Sequential structures***
- ⊕ ***Applications of the sequential structures***
  - latches, registers, counters
- ⊕ ***State machines***
- ⊕ ***Modularity and parameterization of modules***
- ⊕ ***Testbenches***

# State machines

⊕ State machine – synchronous sequential system specified by:

- set of states
- **set of transitions** (oriented) between these states
- **set of transition conditions** (logic expressions based on state machine inputs)
- set of equations that specifies output values

State machine transition diagram

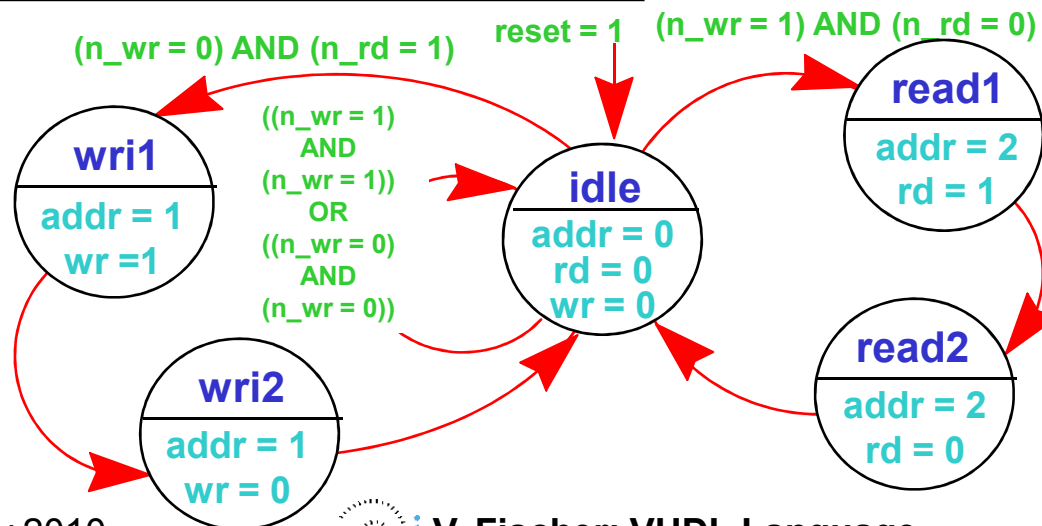

Inputs:

- reset
- n\_wr
- n\_rd

Outputs:

- addr(1..0)
- rd
- wr

## State machine description in VHDL (1/4)

- ⊕ **State machine states** – enumerated data type:

```
TYPE rw_states IS (idle, wr1, wr2, read1, read2);
```


- ⊕ The current state is represented by a SIGNAL, values of this signal are enumerated – defined by the user, the name of this signal will represent the **machine name**

```
SIGNAL sm_rw : rw_states;
```

- ⊕ To determine **the next state**, use the CASE structure (remember that the state machine is a sequential structure), which is inside the structure IF ... THEN awaiting for the rising clock edge
- ⊕ To determine **the outputs**, use conditional assignments or selective assignments

# State machine description in VHDL (2/4)

## ⊕ State machine states

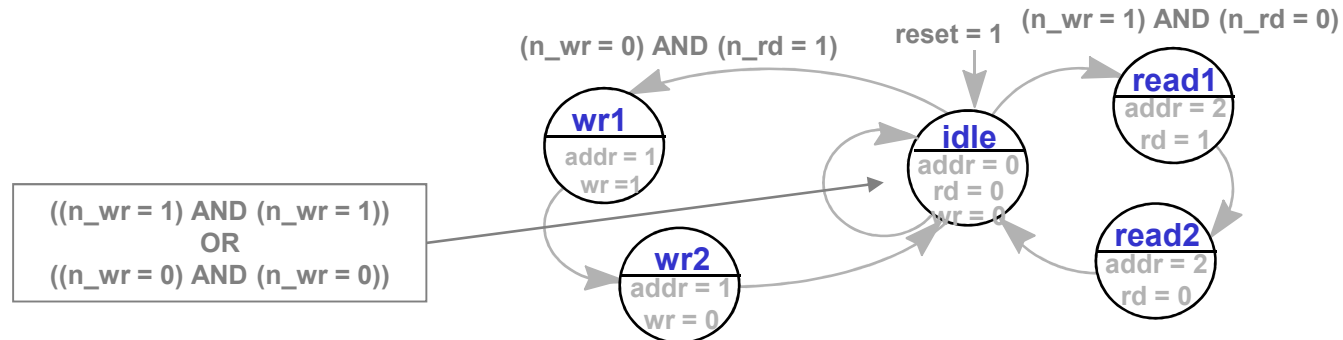

```
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.ALL;

ENTITY machine IS
PORT (clk, reset, n_rd, n_wr : IN std_logic;
      addr : OUT std_logic_vector(1 DOWNTO 0);
      rd, wr : OUT std_logic);
END machine;

ARCHITECTURE behav OF machine IS
  TYPE rw_states IS (idle, wr1, wr2, read1, read2);
  SIGNAL sm_rw : rw_states;
```

*Enumerated type*

to be continued ...

1

# State machine description in VHDL (3/4)


```

BEGIN
PROCESS(reset, clk)
BEGIN
  IF reset = '1' THEN
    sm_rw <= idle;
  ELSIF rising_edge(clk) THEN
    CASE sm_rw IS
      WHEN idle =>
        IF n_wr = '0' AND n_rd = '1' THEN
          sm_rw <= wr1;
        ELSIF n_wr = '1' AND n_rd = '0' THEN
          sm_rw <= read1;
        END IF;
      WHEN wr1 =>
        sm_rw <= wr2;
      WHEN wr2 =>
        sm_rw <= idle;
      WHEN read1 =>
        sm_rw <= read2;
      WHEN read2 =>
        sm_rw <= idle;
      WHEN OTHERS =>
        sm_rw <= idle;
    END CASE;
  END IF;
END PROCESS;

```

⊕ Specification of transitions - inside the PROCESS

Asynchronous reset

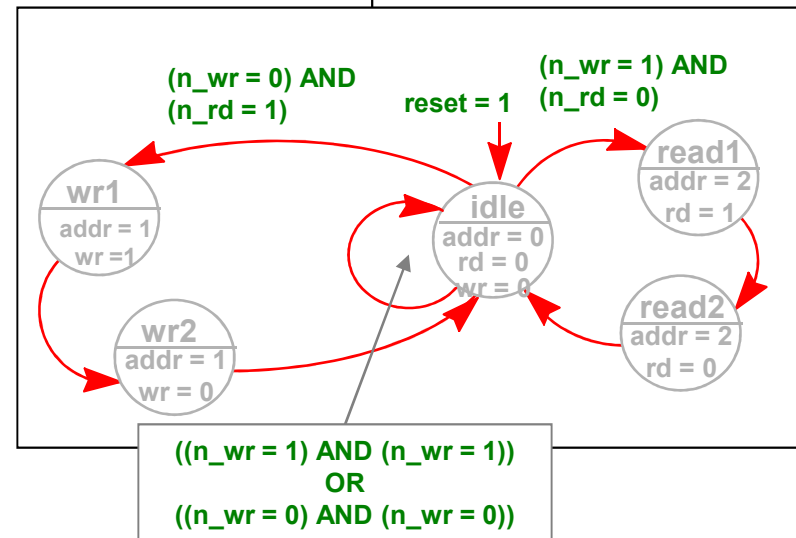

to be continued ...


2






# State machine description in VHDL (4/4)
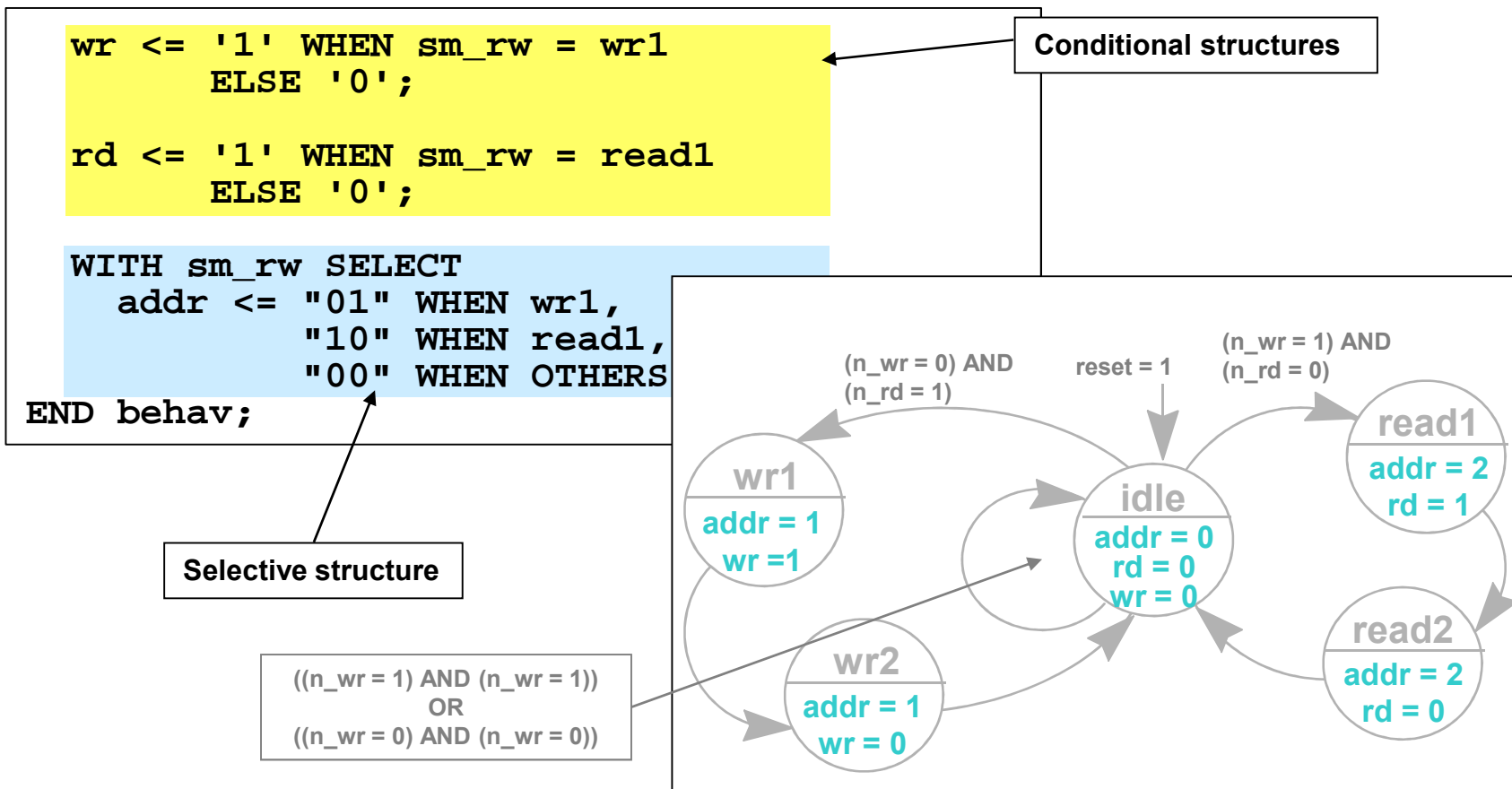
## ⊕ Output specification (concurrent structures)




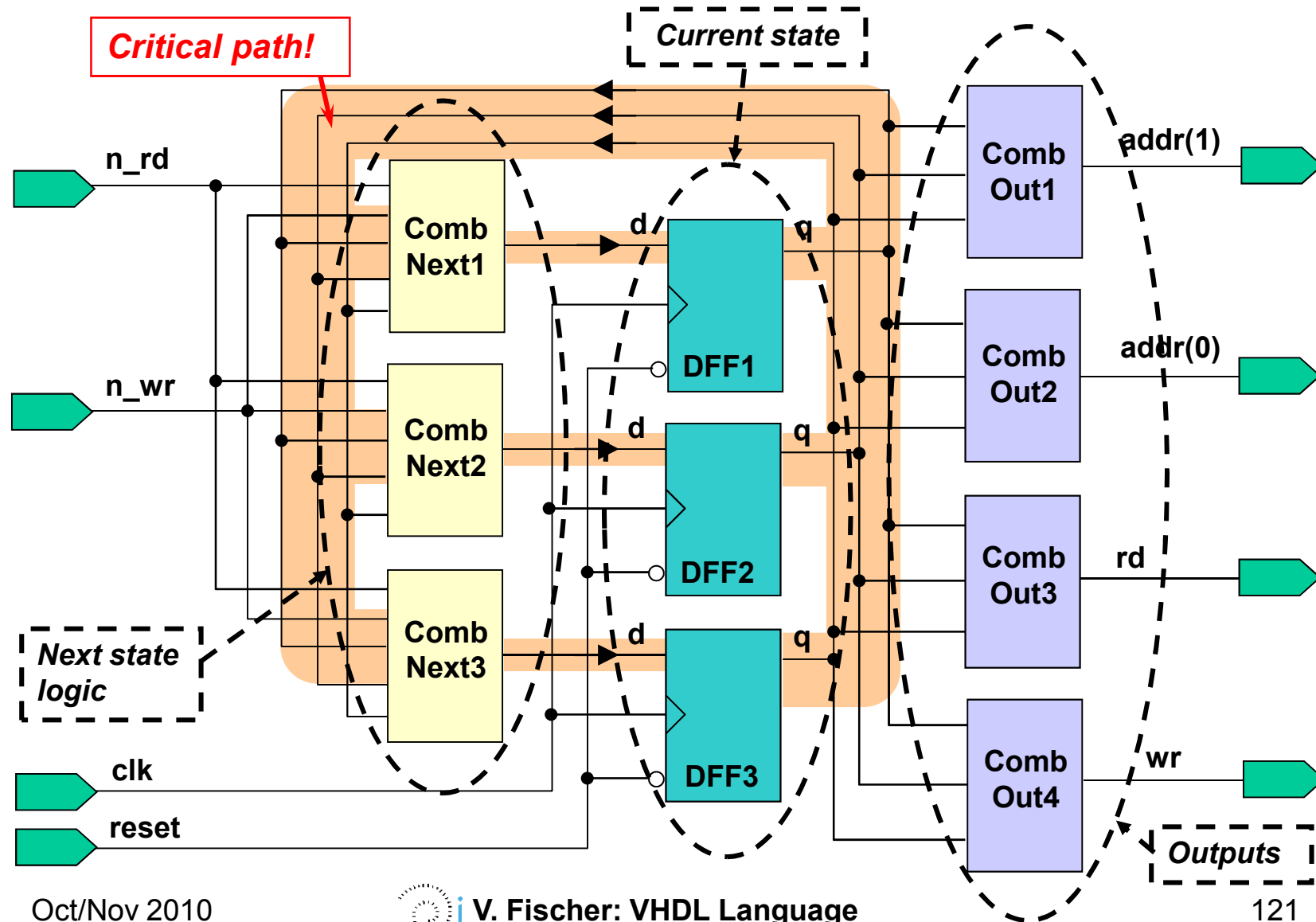
# State machine implementation in hardware (1/3)



## State machine implementation in hardware(2/3)

- ⊕ **If the critical path delay is longer than the clock period**, the machine can enter into a undetermined state where it will stay **blocked forever!**

### Solutions:


- **Reduce the clock frequency**
- **Simplify the combinatorial logic**, which determines the next state (e. g. by using "one hot" coding style, see later)

- ⊕ The state machine can be also blocked if the input signals change **near the rising edge of the clock signal** (flip-flop Setup & Hold time violation)

### Solution:


- **Synchronize inputs** with the clock signal using additional flip-flop for each input – necessary!
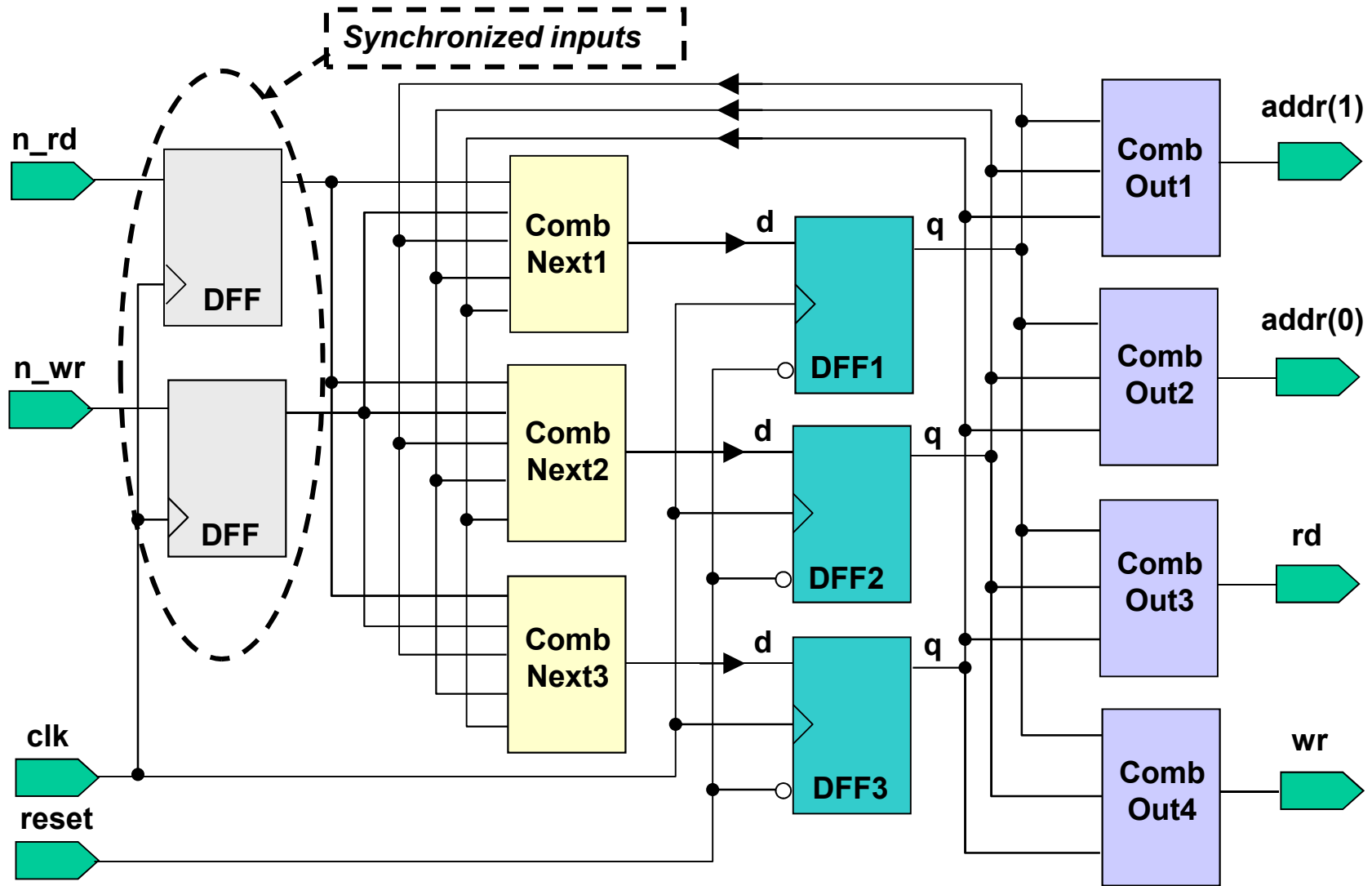
# State machine implementation in hardware (3/3)




# State machine coding styles

## ⊕ Machines with encoded states

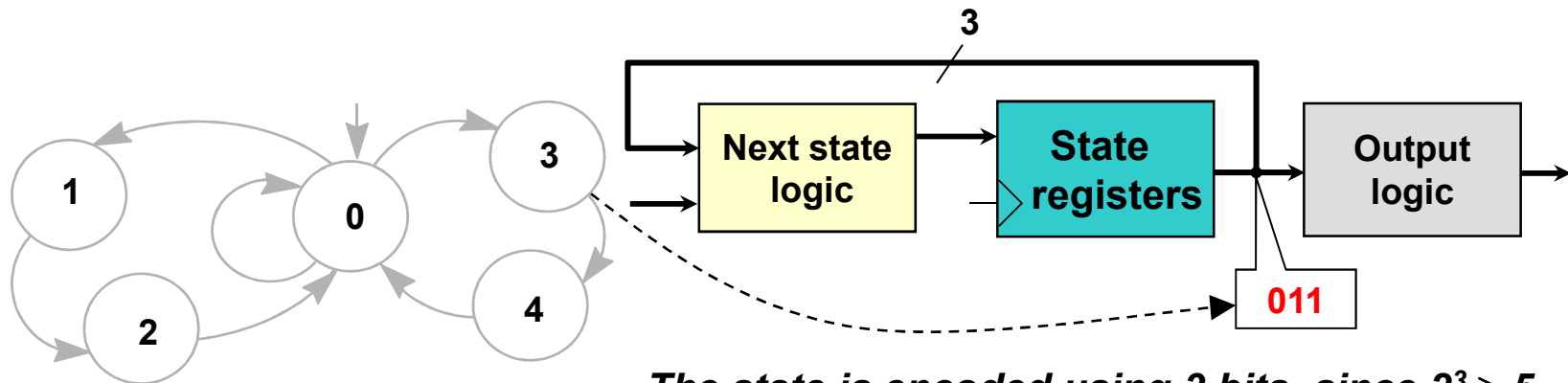

*The state is encoded using 3 bits, since  $2^3 \geq 5$*
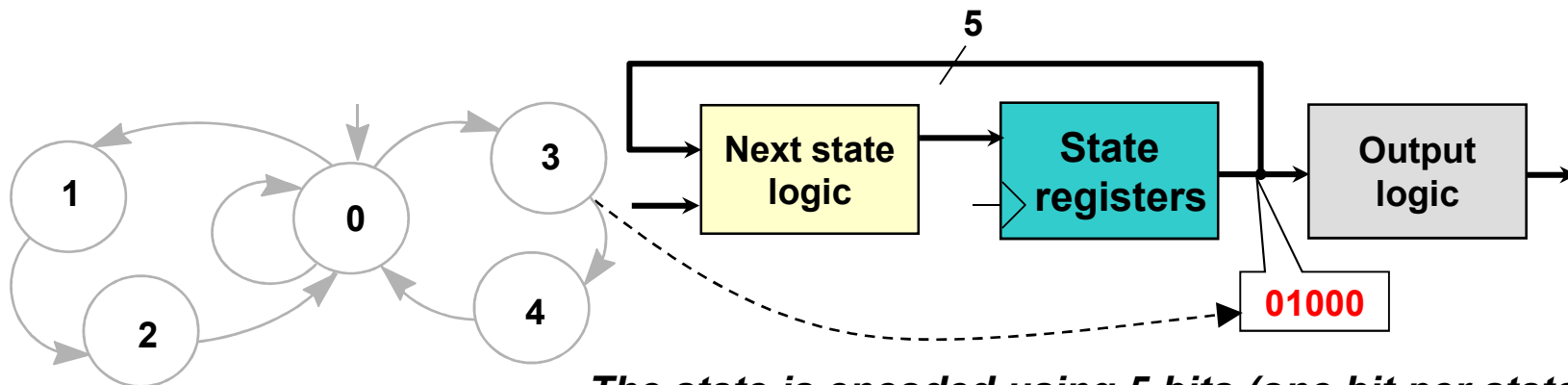
## ⊕ Machines with decoded states ("one-hot" coding style)



*The state is encoded using 5 bits (one bit per state)*

# Machines with decoded states (one-hot style)

## ⊕ Disadvantage

- **one register per state**
  - more registers are needed than for machines with encoded states


## ⊕ Advantages

- **next state logic has less inputs** (one bit per state)
  - less signals means easier routing
- **combinatorial logic** (next state logic and output logic) is **reduced**
  - reduction of the combinatorial logic shortens critical path and increases the machine speed


Note: The type of the state machine coding style is selected by a compiler parameter and not at the VHDL level

# Types of state machines


## ⊕ Moore state machine

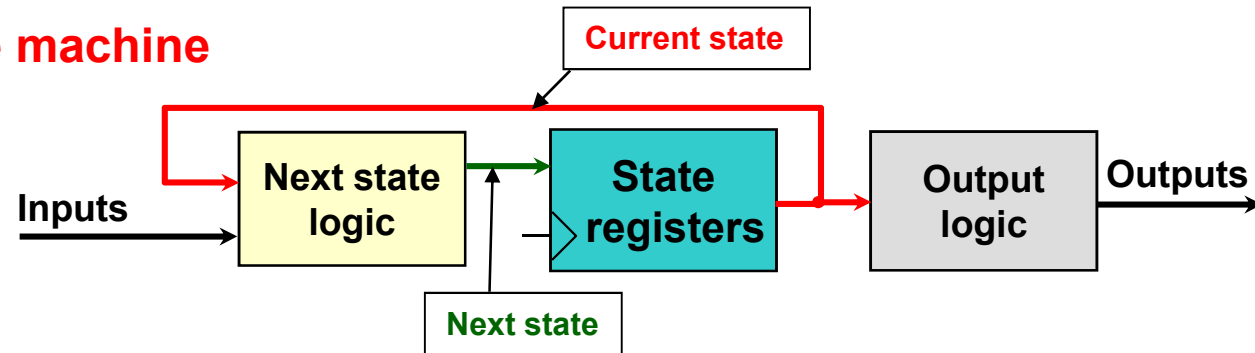

## ⊕ Mealy state machine

 
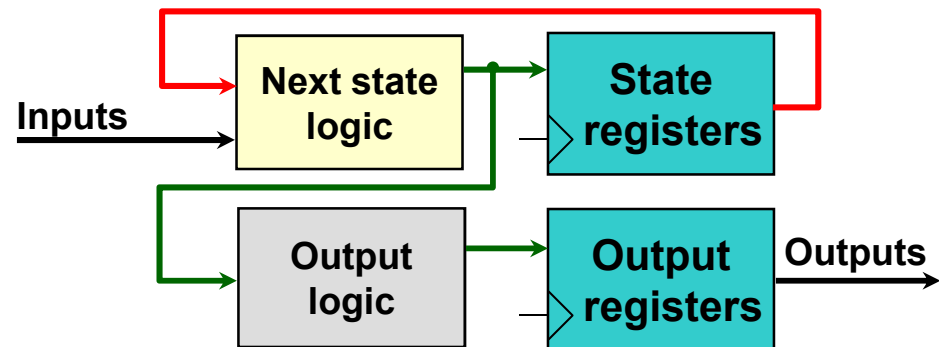
## ⊕ RNS (registered next state ) state machine



# Moore state machine

## ⊕ Principle

- Outputs depend only on the current state

## ⊕ Advantages

- Easy to describe in VHDL (only one CASE structure needed)
- Outputs are valid during the current state
- Output equations are simple, because they depend only on the current state
- Routing is simpler, because inputs have only one destination (the next state logic)

## ⊕ Disadvantage

- Combinatorial output signals can contain glitches



# Moore state machine (cont.)

## Example

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.ALL;

ENTITY machine IS
PORT (clk, reset, n_rd, n_wr : IN std_logic;
      addr : OUT std_logic_vector(1 DOWNTO 0);
      rd, wr : OUT std_logic);
END machine;

ARCHITECTURE behav OF machine IS
TYPE rw_states IS (idle, wr1, wr2, read1, read2);
SIGNAL sm_rw : rw_states;

BEGIN
PROCESS(reset, clk)
BEGIN
IF reset = '1' THEN
sm_rw <= idle;
ELSIF rising_edge(clk) THEN
CASE sm_rw IS
WHEN idle =>
IF n_wr = '0' AND n_rd = '1' THEN
sm_rw <= wr1;
ELSIF n_wr = '1' AND n_rd = '0' THEN
sm_rw <= read1;
END IF;
WHEN wr1 =>
sm_rw <= wr2;
WHEN wr2 =>
sm_rw <= idle;
WHEN read1 =>
sm_rw <= read2;
WHEN read2 =>
sm_rw <= idle;
WHEN OTHERS =>
sm_rw <= idle;
END CASE;
END IF;
END PROCESS;

```

```

wr <= '1' WHEN sm_rw = wr1 ELSE
'0';

rd <= '1' WHEN sm_rw = read1 ELSE
'0';


WITH sm_rw SELECT
addr <= "01" WHEN wr1,
"01" WHEN wr2,
"10" WHEN read1,
"10" WHEN read2,
"00" WHEN OTHERS;

END behav;

```

Outputs (slightly delayed) are related to the current state

Glitches!

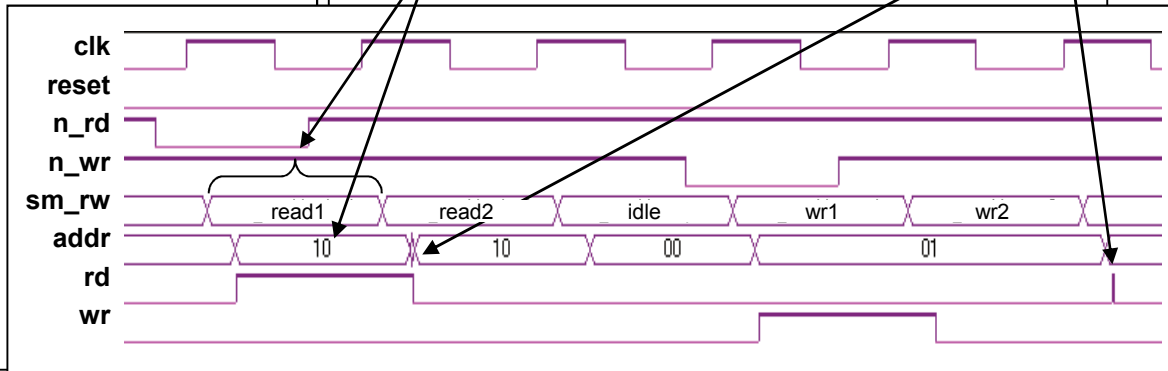



# Mealy state machine

## ⊕ Principle

- Outputs depend on the current state and on the inputs

## ⊕ Advantages

- Easy to describe in VHDL (only one CASE structure needed)
- Outputs respond faster to the input changes
- Less states are needed than for the Moore machine

## ⊕ Disadvantages

- Output equations are more complex, because they depend on the current state and on the inputs
- Routing is more complex, too, because input signals have two destinations (next state logic and output logic)
- Combinatorial output signals can contain glitches

# Mealy state machine (cont.)

## Example

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.ALL;

ENTITY machine IS
PORT (clk, reset, n_rd, n_wr : IN std_logic;
      addr : OUT std_logic_vector(1 DOWNTO 0);
      rd, wr : OUT std_logic);
END machine;

ARCHITECTURE behav OF machine IS
TYPE rw_states IS (idle, write, read);
SIGNAL sm_rw : rw_states;

BEGIN
PROCESS(reset, clk)
BEGIN
IF reset = '1' THEN
sm_rw <= idle;
ELSIF rising_edge(clk) THEN
CASE sm_rw IS
WHEN idle =>
IF n_wr = '0' AND n_rd = '1' THEN
sm_rw <= write;
END IF;
IF n_wr = '1' AND n_rd = '0' THEN
sm_rw <= read;
END IF;
WHEN write =>
sm_rw <= idle;
WHEN read =>
sm_rw <= idle;
WHEN OTHERS =>
sm_rw <= idle;
END CASE;
END IF;
END PROCESS;
```

```
wr <= '1' WHEN ((sm_rw = write)
                AND (n_wr = '0')) ELSE
      '0';


rd <= '1' WHEN ((sm_rw = read)
                AND (n_rd = '0')) ELSE
      '0';

WITH sm_rw SELECT
  addr <= "01" WHEN write,
         "10" WHEN read,
         "00" WHEN OTHERS;

END behav;
```

The output signal changes  
before the state code changes

Glitches!

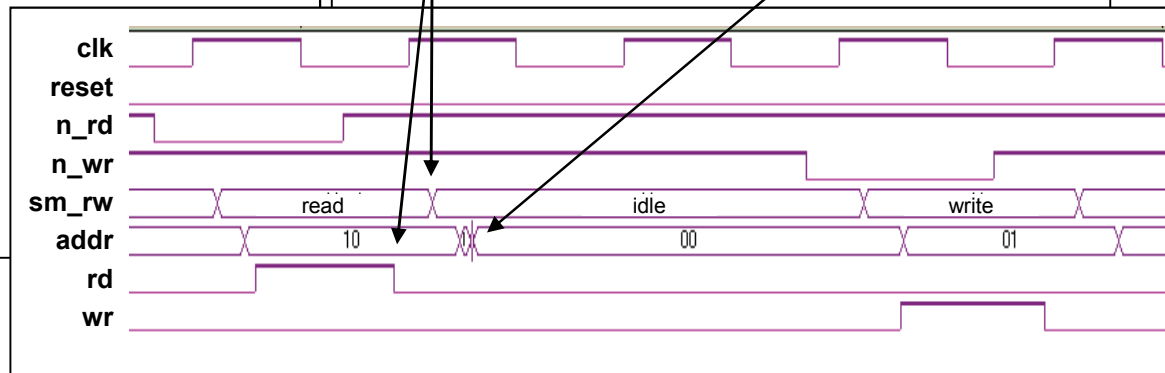

# Elimination of glitches at the state machine output


## ⊕ Solution

- Registering of output signals

## ⊕ Disadvantage

- Outputs are delayed by one period of the clock signal
 
## Example (based on the Moore state machine)



# Elimination of glitches at the output of the Moore and Mealy state machines (cont.)

## Example

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.ALL;

ENTITY machine IS
PORT (clk, reset, n_rd, n_wr : IN std_logic;
      addr : OUT std_logic_vector(1 DOWNTO 0);
      rd, wr : OUT std_logic);
END machine;

ARCHITECTURE behav OF machine IS
TYPE rw_states IS (idle, wr1, wr2, read1, read2);
SIGNAL sm_rw : rw_states;

BEGIN
PROCESS(reset, clk) -- State machine
BEGIN
IF reset = '1' THEN
sm_rw <= idle;
ELSIF rising_edge(clk) THEN
CASE sm_rw IS
WHEN idle =>
IF n_wr = '0' AND n_rd = '1' THEN
sm_rw <= wr1;
END IF;
IF n_wr = '1' AND n_rd = '0' THEN
sm_rw <= read1;
END IF;
WHEN wr1 =>
sm_rw <= wr2;
WHEN wr2 =>
sm_rw <= idle;
WHEN read1 =>
sm_rw <= read2;
WHEN read2 =>
sm_rw <= idle;
WHEN OTHERS =>
sm_rw <= idle;
END CASE;
END IF;
END PROCESS;
PROCESS(clk) -- Output registers
BEGIN

```


```

IF rising_edge(clk) THEN
CASE sm_rw IS
WHEN wr1 =>
addr <= "01";
WHEN wr2 =>
addr <= "01";
WHEN read1 =>
addr <= "10";
WHEN read2 =>
addr <= "10";
WHEN OTHERS =>
addr <= "00";
END CASE;
IF sm_rw = wr1 THEN
wr <= '1';
ELSE
wr <= '0';
END IF;
IF sm_rw = read1 THEN
rd <= '1';
ELSE
rd <= '0';
END IF;
END IF;
END PROCESS;
END behav;

```

Outputs are registered here

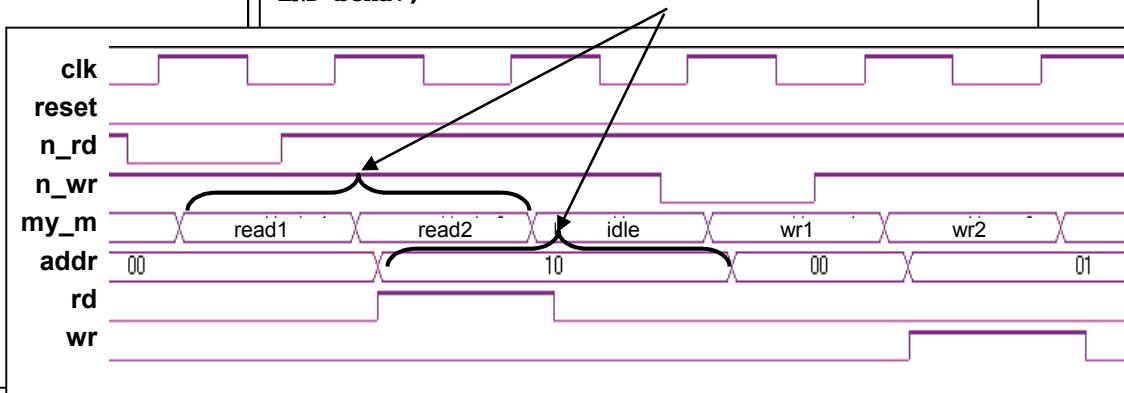Outputs are delayed by one clock period, but without glitches!



# RNS state machine

## ⊕ Principle

- Outputs are decoded from the next state logic and, once decoded, they are registered

## ⊕ Advantages

- Easy to describe in VHDL (only one CASE structure needed)
- Glitches at the outputs are eliminated
- Outputs are not delayed in relationship to the current state (no latency)
- Less states are needed than for the Moore machine

## ⊕ Disadvantages

- The next state logic uses variables and not signals
- The same logic could necessitate more state bits (than for the Mealy machine)

# RNS state machine (cont.)

## Example

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.ALL;

ENTITY machine IS
PORT (clk, reset, n_rd, n_wr : IN std_logic;
      addr : OUT std_logic_vector(1 DOWNTO 0);
      rd, wr : OUT std_logic);
END machine;

ARCHITECTURE behav OF machine IS
TYPE rw_states IS (idle, wr1, wr2, read1, read2);
SIGNAL current_state : rw_states;

BEGIN
PROCESS(reset, clk)
VARIABLE next_state : rw_states;
BEGIN
current_state <= next_state;
IF reset = '1' THEN
next_state := idle;
ELSIF (clk'event AND clk = '1') THEN
CASE current_state IS
WHEN idle =>
IF n_wr = '0' AND n_rd = '1' THEN
next_state := wr1;
END IF;
IF n_wr = '1' AND n_rd = '0' THEN
next_state := read1;
END IF;
END IF;
WHEN ecr1 =>
next_state := wr2;
WHEN ecr2 =>
next_state := idle;
WHEN lec1 =>
next_state := read2;
WHEN lec2 =>
next_state := idle;
WHEN OTHERS =>
next_state := idle;
END CASE;
END PROCESS;


```

```

IF next_state = wr1 THEN
wr <= '1';
ELSE
wr <= '0';
END IF;
IF next_state = read1 THEN
rd <= '1';
ELSE
rd <= '0';
END IF;
CASE next_state IS
WHEN wr1 =>
addr <= "01";
WHEN wr2 =>
addr <= "01";
WHEN read1 =>
addr <= "10";
WHEN read2 =>
addr <= "10";
WHEN OTHERS =>
addr <= "00";
END CASE;
END IF;
END PROCESS;
END behav;

```

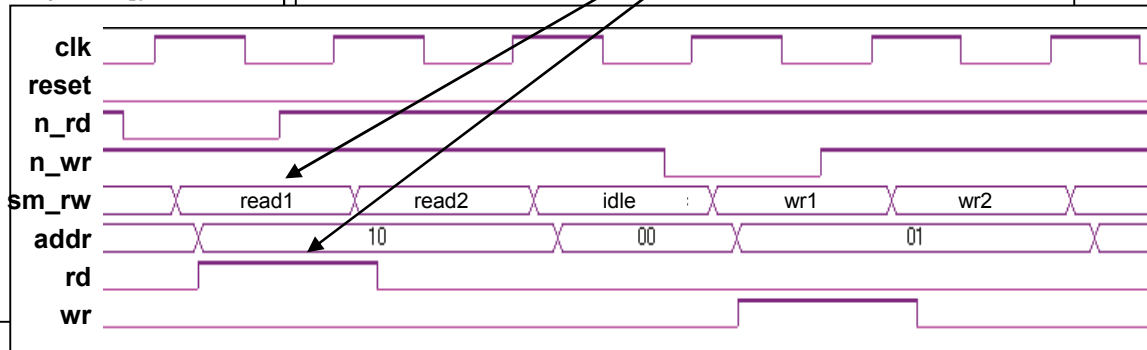The output changes in the same time as the state and there are no glitches!



# Contents


- ⊕ ***Introduction***
- ⊕ ***VHDL basics***
- ⊕ ***Concurrent structures***
- ⊕ ***Applications of the concurrent structures***
  - decoders, parity checkers, multiplexers, arithmetic logic units, tri-state outputs, bi-directional inputs/outputs
- ⊕ ***Sequential structures***
- ⊕ ***Applications of the sequential structures***
  - latches, registers, counters
- ⊕ ***State machines***
- ⊕ ***Modularity and parameterization of modules***
- ⊕ ***Testbenches***



# Hierarchical design in VHDL

- ⊕ Needs declaration and instantiation of the components

Example :

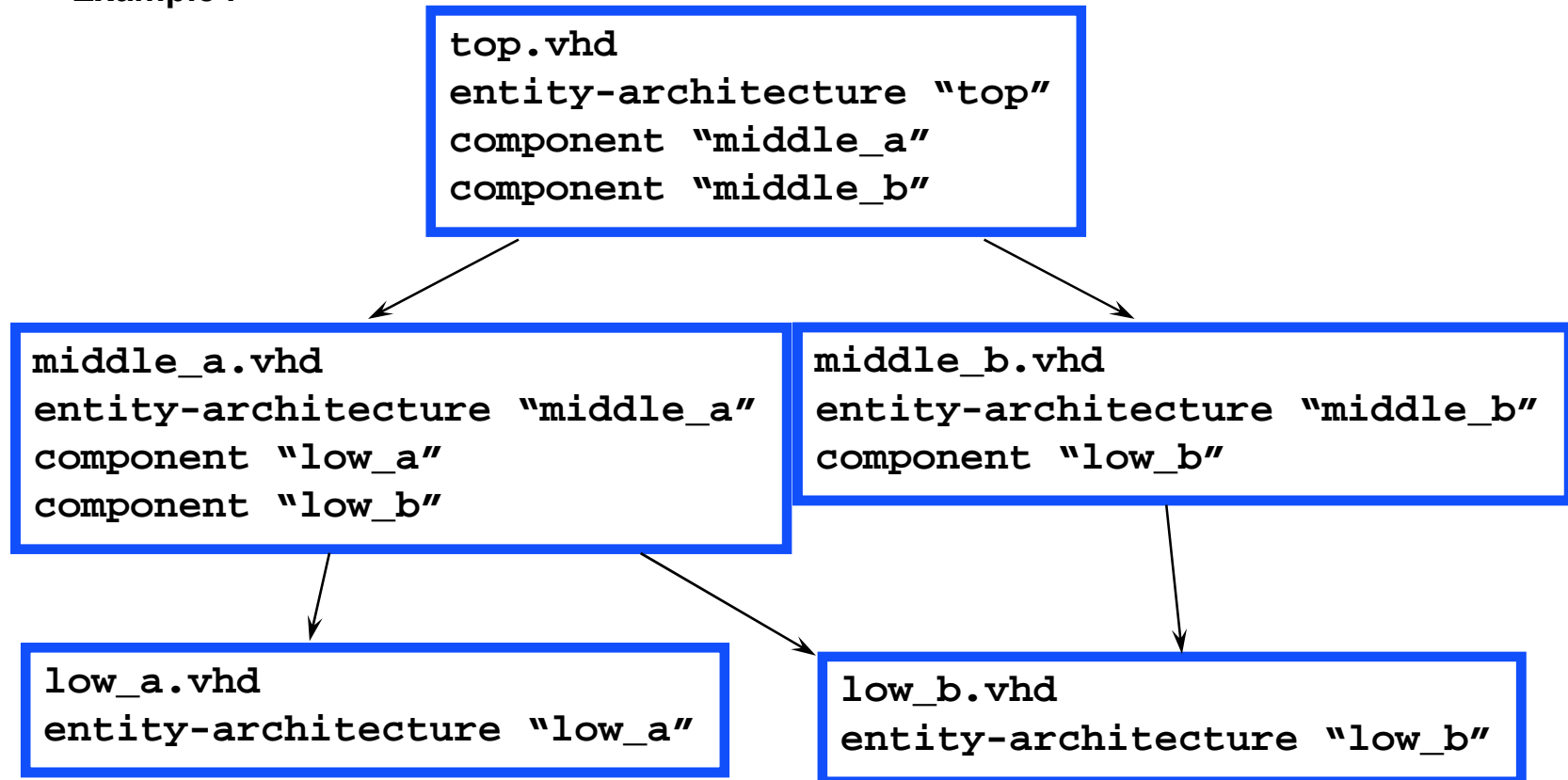



# Declaration and instantiation of the component

## ⊕ Component declaration

- It is used to declare the port types and data types of the lower level component

```
COMPONENT <low_level_component_name> IS
PORT (<port_name> : <port_type> <data_type>; ← Semicolon
      :
      (<port_name> : <port_type> <data_type> <data_type> ← No semicolon
      );
END COMPONENT;
```

## ⊕ Component instantiation

- It is used to associate the lower-level component ports with current level signals

```
<instance_name> : <low_level_component_name>
PORT MAP (<low_level_port_name> => <current_level_signal_name>, ← comma
          :
          <low_level_port_name> => <current_level_signal_name>
          ); ← No comma
```

## Advantages of the hierarchical design

- ⊕ Each team member can design **modules** (components) **independently (in separated files)**
- ⊕ The components can be **reused later** by other team members
- ⊕ Hierarchical design enhances **modularity and portability** of the projects
- ⊕ Hierarchical design simplifies the possibility **to implement and to test various versions of the same module**
- ⊕ Compilation options can be applied globally or per component - the design can be **locally optimized!**
- ⊕ **More hierarchical levels mean more flexibility!**

## Two modularity approaches

### ⊕ Design modularity optimization for the placement and routing (P/R) - searching the optimum size of the module

- If the modules are too small, the placement and routing is not easier (it is the same as for the one-module design)
- If the modules are too big, the placement and routing can be even more difficult
- Optimum module size for the FPGAs : 40 – 60 Logic Cells

### ⊕ Design modularity optimization for the performance – searching modules with optimal cost (area) and performance (speed)

- Area-critical and speed-critical modules can be separated and optimized independently

# Component (module) parameterization

- ⊕ Enables to enhance the module **portability (universality)**
- ⊕ Brings **huge flexibility** to the component description
- ⊕ Constitutes the principle of the **LPM library** (Library of Parameterized Modules), which is used by vendors to propose hardware-optimized macrofunctions
- ⊕ The parameterization is realized by the **GENERIC structure**, example:

```
ENTITY multiplexer IS
  GENERIC (WIDTH : integer := 4);
  PORT(sel : IN bit;
        a, b : IN bit_vector(WIDTH-1 DOWNTO 0);
        c : OUT bit_vector(WIDTH -1 DOWNTO 0));
END multiplexer;
ARCHITECTURE a_mux OF multiplexer IS
BEGIN
  c <= a WHEN sel = '0' ELSE b;
END a_mux;
```

Default value

## Component instantiation:

```
mux_inst: multiplexer GENERIC MAP (WIDTH => 8)
  PORT MAP(sel => selh, a => ah, b => bh, c => ch);
```

Current value

# Contents

- ⊕ ***Introduction***
- ⊕ ***VHDL basics***
- ⊕ ***Concurrent structures***
- ⊕ ***Applications of the concurrent structures***
  - decoders, parity checkers, multiplexers, arithmetic logic units, tri-state outputs, bi-directional inputs/outputs
- ⊕ ***Sequential structures***
- ⊕ ***Applications of the sequential structures***
  - latches, registers, counters
- ⊕ ***State machines***
- ⊕ ***Modularity and parameterization of modules***
- ⊕ ***Testbenches***

# Testbenches

- ⊕ Enable **optimization and automation of the component functionality verification**
  
- ⊕ **VHDL testbench structure:**
  - The entity does not contain input/outputs (however, the **GENERIC** structure can be used to define the clock signal period)
  - The component to test (DUT – Design Under Test) is declared and instantiated in the testbench architecture
  - Each component input signal is associated to a stimulator – an internal signal of the testbench architecture
  - The stimuli are generated using the **PROCESS**
  
- ⊕ Testbenches use **all the potential of the VHDL language!**

# Clock signal generation

- ⊕ In the declaration part of the architecture:

```
-- Clock period definition
CONSTANT ClockPeriod : TIME := 10 ns;
```

- ⊕ **Method 1** of the clock signal generation:

```
-- Clock signal generation
clock <= NOT clock AFTER ClockPeriod / 2;
```

- ⊕ **Method 2** of the clock signal generation :

```
-- Clock signal generation
clock <= NOT clock AFTER ClockPeriod / 2;
Clock_generator: PROCESS
BEGIN
    WAIT FOR (ClockPeriod / 2)
    clock <= '1';
    WAIT FOR (ClockPeriod / 2)
    clock <= '0';
END PROCESS;
```



# Stimuli generation in an absolute time scale

## Example:

```
stimuli : PROCESS
BEGIN
  reset <= '1';
  load  <= '0';
  count_updn <= '0';
  WAIT FOR 100 ns;
  reset <= '0';
  WAIT FOR 30 ns;
  load  <= '1';
  WAIT FOR 20 ns;
  count_updn <= '1';
  WAIT; ←
END PROCESS;
```

The WAIT instruction (without FOR) permits to stop definitively the PROCESS execution, without this instruction, it would restart from the very beginning

# Stimuli generation in a relative time scale

## Example:

```
stimulus1 : PROCESS (clk)
BEGIN
    IF clk'event AND clk = '1' THEN
        tb_count <= tb_count + 1;
    END IF;
END PROCESS;
stimulus2 : PROCESS
BEGIN
    IF (tb_count <= 5) THEN
        reset <= '1';
        load  <= '0';
        count_updn <= '0';
    ELSE
        reset <= '1';
        load  <= '0';
        count_updn <= '0';
        report "Reset done!";
    END IF;
END PROCESS;
```

# Self-checking testbenches

- ✦ Use the *textio* package of the VHDL language

## Example:

```
LIBRARY IEEE;
USE IEEE.std_logic_1164.all;
LIBRARY ieee;
USE IEEE.std_logic_textio.all;
USE STD.textio.all;
ENTITY testbench IS
END testbench;
ARCHITECTURE testbench_arch OF testbench IS
  COMPONENT stopwatch
  PORT (
    clk : IN std_logic;
    reset : IN std_logic;
    strtstop : IN std_logic;
    tenthsout : OUT std_logic_vector (9 DOWNTO 0);
    onesout : OUT std_logic_vector (6 DOWNTO 0);
    tensout : OUT std_logic_vector (6 DOWNTO 0)
  );
END COMPONENT;
SIGNAL clk : std_logic;
SIGNAL reset : std_logic;
SIGNAL strtstop : std_logic;
SIGNAL tenthsout : std_logic_vector (9 DOWNTO 0);
SIGNAL onesout : std_logic_vector (6 DOWNTO 0);
SIGNAL tensout : std_logic_vector (6 DOWNTO 0);
CONSTANT ClockPeriod : Time := 60 ns;
FILE RESULTS: TEXT IS OUT "results.txt";
SIGNAL i: std_logic;

BEGIN
  uut : stopwatch -- component instantiation
  PORT MAP (
    clk => clk,
    reset => reset,
    strtstop => strtstop,
    tenthsout => tenthsout,
    onesout => onesout,
    tensout => tensout
  );
```

```
stimulus: PROCESS -- stimuli
  BEGIN
    reset <= '1';
    strtstop <= '1';
    WAIT FOR 240 ns;
    reset <= '0';
    strtstop <= '0';
    WAIT FOR 5000 ns;
    strtstop <= '1';
    WAIT FOR 8125 ns;
    strtstop <= '0';
    WAIT FOR 500 ns;
    strtstop <= '1';
    WAIT FOR 875 ns;
    reset <= '1';
    WAIT FOR 375 ns;
    reset <= '0';
    WAIT FOR 700 ns;
    strtstop <= '0';
    WAIT FOR 550 ns;
    strtstop <= '1';
  END PROCESS stimulus;

clock: PROCESS -- clock signal
  BEGIN
    clk <= '1';
    WAIT FOR 100 ns;
    LOOP
      WAIT FOR (ClockPeriod / 2);
      clk <= NOT clk;
    END LOOP;
  END PROCESS clock;
```

Results will be written to this file

à suivre ...

# Self-checking testbenches (cont.)

## ⊕ Example – cont.

```
check_results : PROCESS -- verification of results
  VARIABLE tmp_tenthsout: std_logic_vector(9 DOWNTO 0);
  VARIABLE l: line;
  VARIABLE good_val, good_number, errordet: boolean;
  VARIABLE r : real;
  VARIABLE vector_time: time;
  VARIABLE space: character;
  FILE vector_file: TEXT IS IN "values.txt";
BEGIN
  WHILE NOT ENDfile(vector_file) LOOP
    readline(vector_file, l);
    read(l, r, good => good_number);
    NEXT WHEN NOT good_number;
    vector_time := r * 1 ns;
    IF (now < vector_time) THEN
      WAIT FOR vector_time - now;
    END IF;
    read(l, space);
    read(l, tmp_tenthsout, good_val);
    ASSERT good_val REPORT "bad tenthsoutvalue";
    WAIT FOR 10 ns;
    IF (tmp_tenthsout /= tenthsout) THEN
      ASSERT errordet REPORT "vector mismatch";
    END IF;
  END LOOP;
  WAIT;
END PROCESS check_results;
END testbench_arch;
```

Input file specification

Reading the file

Warning

```
-- The file "values.txt" containing test vectors
-- and results
0 1111111110
340 1111111110
400 1111111101
460 1111111011
520 1111110111
580 1111101111
640 1111011111
700 1110111111
760 1101111111
820 1011111111
880 0111111111
940 1111111110
1000 1111111110
1060 1111111101
1120 1111111011
1180 1111110111
1240 1111101111
1300 1111011111
1360 1110111111
1420 1101111111
1480 1011111111
1540 0111111111
1600 1111111110
1660 1111111110
1720 1111111101
1780 1111111011
```

Error message